

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations July-2022

ELECTRONIC DEVICES AND CIRCUITS

(Common to EEE & ECE)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

- 1 a** Analyze the current components in a PN diode and develop the expression for diode current equation. **L6 8M**
- b** When a reverse bias is applied to a germanium PN junction diode, the reverse saturation current at room temperature is $0.3\mu\text{A}$. Determine the current flowing in the diode when 0.15V forward bias is applied at room temperature. **L5 4M**

OR

- 2 a** Draw and explain the V-I characteristics of Zener diode. **L2 6M**
- b** Explain Positive and Negative Diode Clippers with neat waveforms. **L2 6M**

UNIT-II

- 3 a** With neat circuit diagram and waveforms, illustrate the construction and working of Bridge rectifier. **L2 5M**
- b** Draw the circuit diagram of Full wave rectifier with inductor filter and illustrate its operation. Also derive the expression for ripple factor. **L1 7M**

OR

- 4 a** Explain the working principle of CLC or π section filter and also derive the expression for ripple factor. **L2 6M**
- b** Demonstrate the working and characteristics of UJT with neat diagram. **L2 6M**

UNIT-III

- 5 a** Explain the operation of NPN transistor with neat diagram. **L2 6M**
- b** Illustrate the Input and Output characteristics of BJT in CC Configuration. Also Obtain the expression for Output collector current equation for a Transistor in CC configuration. **L2 6M**

OR


- 6** Interpret the operation and characteristics of n-channel depletion type MOSFET with diagram. **L2 12M**

UNIT-IV

- 7 a Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. L2 7M
- b List the different types of Biasing a Transistor and explain the fixed bias of a Transistor. L4 5M

OR

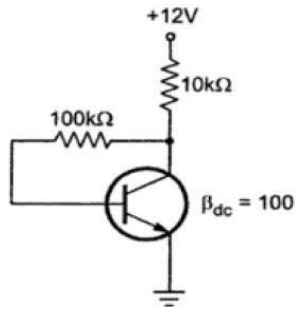- 8 a Explain Thermal Runaway and Thermal Resistance. L2 6M
- b Solve for the Q-point values for the circuit shown in the Fig. L5 6M



UNIT-V

- 9 a Determine the parameters A_i , R_i , A_v and R_o of Common Collector Amplifier using simplified hybrid model analysis. L5 6M
- b A voltage source of internal resistance, $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$. The CE h parameters are $h_{fe} = 60$, $h_{ie} = 1200\Omega$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Solve A_i , R_i , A_v and R_o using approximate analysis. L3 6M

OR

- 10 A CE amplifier is driven by a voltage source of internal resistance $R_s = 800\Omega$ and the load impedance of $R_L = 1000\Omega$. The h-parameters are $h_{ic} = 1k$, $h_{fe} = 50$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Find current gain, voltage gain, input impedance and output impedance using exact analysis and approximate analysis. L1 12M

*** END ***