

Reg. No:

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Supplementary Examinations July-2022

POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Explain the switching characteristics of BJT. L1 6M
b Write short note on Turn on methods of SCR. L2 6M

OR

- 2 a Describe input and transfer characteristics of an IGBT. L1 8M
b Define Latching current and Holding current. L2 4M

UNIT-II

- 3 Explain the operation of single phase full wave midpoint converter with RL load. L3 12M
Also derive the output voltage and output current equations.

OR

- 4 What is a freewheeling diode? Draw single phase semi converter with RLE load L3 12M
with freewheeling diode and explain the operation with necessary output waveforms.

UNIT-III

- 5 a Give the difference between discontinuous mode and continuous mode of operation. L1 6M
b Give the difference between midpoint and bridge type converters L1 6M

OR

- 6 Explain the operation of three phase dual converter with non-circulating current type. L3 12M

UNIT-IV

- 7 a What is meant by ac voltage controllers and what are the different types? L2 8M
b List the applications of ac voltage controller. L1 4M

OR

- 8 Explain about the 1 – Ø AC voltage controller with RL loads with neat diagram L3 12M

UNIT-V

- 9 Describe different types of pulse width modulation techniques (PWM) inverter. L3 12M

OR

- 10 Describe the working of single phase full bridge inverter with neat waveforms. L3 12M

*** END ***