

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

**B. Tech II Year I Semester Supplementary Examinations December-2021
ELECTRONIC DEVICES**

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | |
|---|--|----|----|
| 1 | a Define barrier potential. | L1 | 2M |
| | b Compare half wave rectifier and Full wave rectifier. | L2 | 2M |
| | c What do you mean by Punch through Effect? | L1 | 2M |
| | d Draw the generalized hybrid model for BJT amplifier. | L2 | 2M |
| | e Define Pinch off Voltage | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | |
|---|---|----|----|
| 2 | a What is a PN Junction? Explain the formation of depletion layer in a PN junction. | L2 | 5M |
| | b Derive the Diode Current Equation. | L1 | 5M |

OR

- | | | | |
|---|---|----|----|
| 3 | a Mention the importance of Diffusion capacitance. | L1 | 2M |
| | b Derive the expression for Diffusion capacitance of a PN Junction Diode. | L3 | 8M |

UNIT-II

- | | | | |
|---|---|----|----|
| 4 | a Draw the circuit diagram of Full wave rectifier and explain its operation with the help of waveforms. | L2 | 5M |
| | b Derive the expressions for Ripple Factor and Efficiency of Full Wave Rectifier. | L1 | 5M |

OR

- | | | | |
|---|---|----|----|
| 5 | a Draw and discuss the VI characteristics of a Zener Diode. | L2 | 5M |
| | b Derive the expression for ripple factor of inductor filter. | L3 | 5M |

UNIT-III

- | | | | |
|---|---|----|----|
| 6 | a Discuss the operation of NPN transistor with diagram. | L2 | 5M |
| | b If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current. | L3 | 5M |

OR

- | | | | |
|---|--|----|-----|
| 7 | Derive the condition for Thermal Stability to avoid thermal runaway. | L3 | 10M |
|---|--|----|-----|

UNIT-IV

- | | | | |
|---|---|----|----|
| 8 | a Determine the parameters A_i , R_i , A_v and R_0 of Emitter Follower using simplified hybrid model analysis. | L3 | 5M |
| | b voltage source of internal resistance $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$. The CE h parameters are $h_{fe} = 60$, $h_{ie} = 1200\Omega$, $h_{oe} = 25\mu\text{A/V}$ and $h_{re} = 2 \times 10^{-4}$. Compute A_i , R_i , A_v and R_0 using approximate analysis. | L3 | 5M |

OR


- 9 a Draw the circuit diagram of a single stage RC coupled Amplifier and discuss the steps used for designing it. L2 5M
- b Determine Voltage Gain, Current Gain, Input resistance and Output resistance for a CE amplifier using NPN transistor with $h_{ie} = 1200\Omega$, $h_{re} = 0$, $h_{fe} = 36$ and $h_{oe} = 2 \times 10^{-6}$ mhos, $R_L = 2.5k\Omega$ and $R_S = 500\Omega$ (neglect the effect of biasing circuit). L3 5M

UNIT-V

- 10 a Describe the construction and working principle of N-channel JFET. L2 5M
- b Mention the applications of JFET. L1 5M

OR

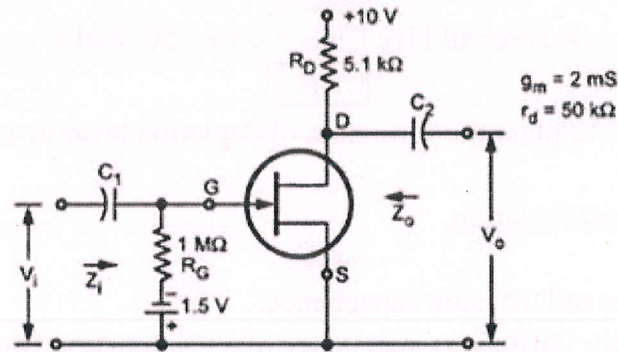- 11 a Draw and explain the small signal model of FET at low frequency. L1 4M
- b For the circuit shown in Fig. determine input impedance, output impedance and voltage gain. L4 6M



END