

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations December-2021

ELECTRICAL CIRCUITS-II

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | |
|---|---|----|----|
| 1 | a Write the voltage and current relationship in star connected system. | L2 | 2M |
| | b What is the transient response of RL series circuit with dc excitation? | L2 | 2M |
| | c Define graph. | L2 | 2M |
| | d Define Z- Parameters. | L2 | 2M |
| | e Define Laplace transform of a function. | L2 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | |
|---|--|----|----|
| 2 | a Derive the relationship between Phase and Line voltages, currents in delta-connected load. | L2 | 5M |
| | b A balanced star connected load of $(4+j3) \Omega$ per phase is connected to a balanced 3 ϕ 400v supply. Find a) active power b) reactive power c) Apparent power. | L3 | 5M |

OR

- | | | | |
|---|--|----|----|
| 3 | a Explain reactive power measurement in balanced three phase load using single watt meter | L2 | 5M |
| | b A balanced delta connected load of $(4+j3) \Omega$ per phase is connected to a balanced 3 ϕ 440v supply.. Find i) active power ii) reactive power iii) Apparent power | L3 | 5M |

UNIT-II


- | | | | |
|---|---|----|----|
| 4 | a Derive the transient response of an RL circuit with DC excitation. | L2 | 5M |
| | b A series RL circuit with $R=30\Omega$ and $L=15H$ has a constant voltage $V=60V$ applied at $t=0$. Determine the current I, the voltage across the resistor and across the inductor. | L3 | 5M |

OR

- | | | | |
|---|---|----|----|
| 5 | a Derive the transient response of an RL circuit with AC excitation. | L2 | 5M |
| | b Derive the transient response of an RLC circuit with DC excitation. | L3 | 5M |


UNIT-III

- | | | | |
|---|--|----|-----|
| 6 | Determine mesh currents for the following network using network topology | L3 | 10M |
|---|--|----|-----|

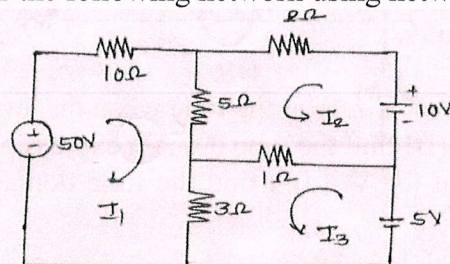


OR

- | | | | |
|---|--|----|----|
| 7 | a Find the cutset matrix for the followings? | L3 | 6M |
|---|--|----|----|

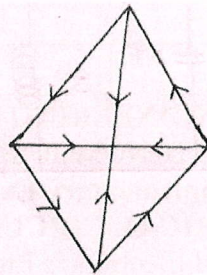

b Write the procedure to draw the dual network and find dual network for the followings

L2 4M

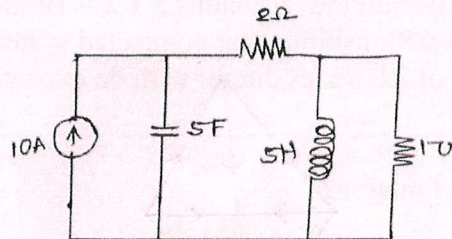

UNIT-IV


8 a Derive the expressions for Z-parameters in terms of ABCD parameters.

L2 6M

b Find the Z - parameters for the resistance network shown in figure

4M

L3

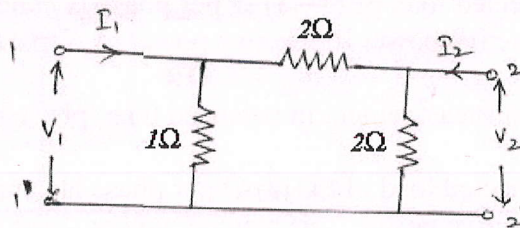

OR

9 a Prove the g parameters can be obtained from the z parameters as

L2 5M

$$g_{11} = \frac{1}{z_{11}} \quad g_{12} = \frac{-z_{12}}{z_{11}} \quad g_{21} = \frac{z_{21}}{z_{11}} \quad g_{22} = \frac{\Delta_z}{z_{11}}$$

b Derive the expressions for h-parameters of a two port network?

L2 5M

UNIT-V


10 A 500Ω resistor, a 16mH inductor, and a 25 nF capacitor are connected in parallel which is placed in series with a 2000Ω resistor. Express the impedance of this series combination as a rational function of s.

L3 10M

OR

11 The energy stored in the circuit shown is zero at the time when the switch is closed. (A) find the s- domain expression for I (B) find the time domain expression for i when t > 0. (c) find the s- domain expression for V. (d) find the time domain expression for v when t > 0.

L3 10M

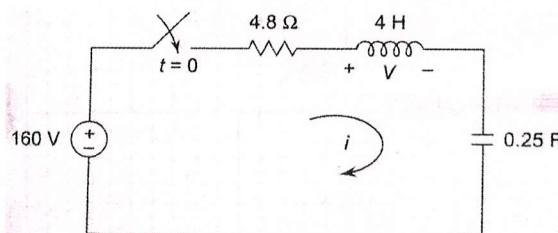

END