

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)
B.Tech II Year I Semester Supplementary Examinations December-2021
BASIC ELECTRICAL & ELECTRONICS ENGINEERING
(Mechanical Engineering)


Time: 3 hours

Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART-A**UNIT-I**

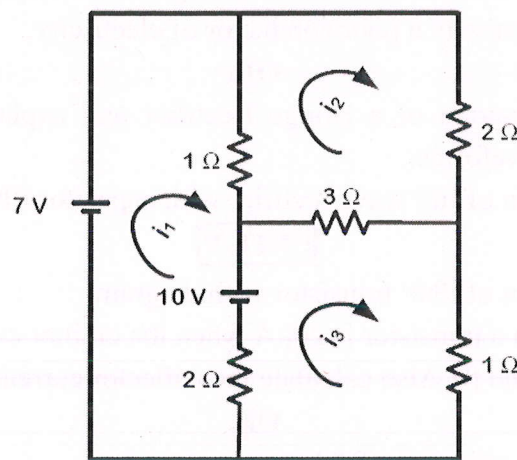- 1 a State and prove Kirchoff's laws with suitable examples. 5M
b Find i_1 , i_2 , i_3 for the given circuit by using Kirchoff's laws? 5M




OR

- 2 Explain about the Star-Delta and Delta-Star transformation. 10M

UNIT-II

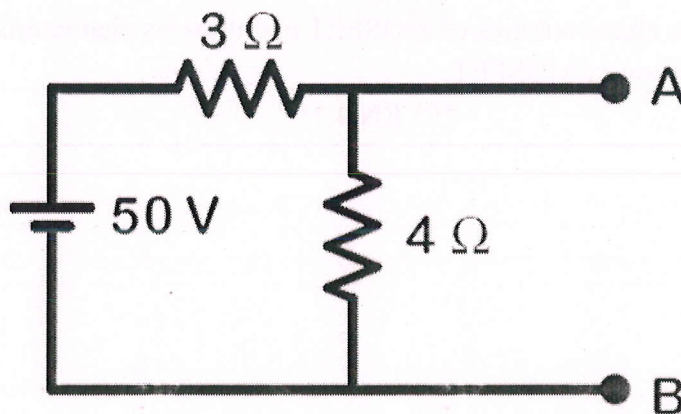- 3 a State Thevenin's theorem. 5M
b Find the Thevenin's equivalent circuit across AB for the circuit shown. 5M



OR

- 4 a Explain in detail about Impedance parameters. 5M
b Briefly discuss about Admittance parameters. 5M

UNIT-III

- 5 a Discuss about the principle of operation of DC motors. 5M
b Calculate the value of torque established by the armature of a 4-pole DC motor having 774 conductors, 2 paths in parallel, 24mwb flux per pole when the total armature current is 50A. 5M

OR

- 6 a Derive EMF equation of a transformer. 6M
b A 100 kVA, 11000/400 V, 50 Hz transformer has 40 secondary turns. Calculate the number of primary turns and primary and secondary currents. 4M

PART-B**UNIT-IV**

- 7 a Distinguish between conductors, semiconductors and insulators. 5M
b Draw the atomic structure of a semiconductor and explain why an intrinsic semiconductor is relatively a poor conductor of electricity. 5M

OR

- 8 a Draw the circuit diagram of a Bridge Rectifier and explain its operation with input and output waveforms. 5M
b Discuss the operation of full wave rectifier with capacitor filter. 5M

UNIT-V

- 9 a Discuss the operation of PNP transistor with diagram. 5M
b If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current. 5M

OR

- 10 a Write notes on early effect of a BJT. 5M
b Describe the region of BJT when it's operating. 5M

UNIT-VI

- 11 a Explain the output characteristics of JFET. 5M
b Explain the transfer characteristics of JFET. 5M

OR

- 12 a Explain the static characteristics of MOSFET and draw its characteristics. 6M
b Write the application of MOSFET. 4M

***** END *****