

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations December-2021

BASIC ELECTRONIC DEVICES

(Common to EEE & ECE)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- | | | | |
|---|--|----|----|
| 1 | a Discuss the Energy bands in intrinsic and extrinsic silicon. | L2 | 6M |
| | b Write notes on carrier transport in semiconductor. | L2 | 6M |

OR

- | | | | |
|---|--------------------------------------|----|----|
| 2 | a Derive the Diode Current Equation. | L1 | 6M |
| | b Write notes on Diode Resistance. | L2 | 6M |

UNIT-II

- | | | | |
|---|---|----|----|
| 3 | a Draw and explain VI characteristics of Tunnel Diode. | L2 | 6M |
| | b Discuss the basic structure and characteristics of TRIAC. | L2 | 6M |

OR

- | | | | |
|---|---|----|----|
| 4 | a With neat diagram, describe the working principle and characteristics of UJT. | L1 | 6M |
| | b Write notes on Photo Transistor. | L2 | 6M |

UNIT-III

- | | | | |
|---|---|----|-----|
| 5 | Derive the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power Input of a Half Wave Rectifier. | L1 | 12M |
|---|---|----|-----|

OR

- | | | | |
|---|---|----|----|
| 6 | a Draw the circuit of capacitor filter and explain its operation. | L1 | 6M |
| | b Derive the expression for ripple factor of HWR and FWR with capacitor filter. | L2 | 6M |

UNIT-IV

- | | | | |
|---|---|----|----|
| 7 | a If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current. | L3 | 8M |
| | b Write notes on early effect of a BJT? | L1 | 4M |

OR

- | | | | |
|---|---|----|----|
| 8 | a Discuss the operation and drain characteristics of n-channel depletion type MOSFET. | L2 | 6M |
| | b Give the comparison between JFET and MOSFET. | L4 | 6M |

UNIT-V

- | | | | |
|---|--|----|----|
| 9 | a Describe Thermistor and Sensistor Compensation Techniques. | L1 | 6M |
| | b Discuss about Thermal Runaway and Thermal Resistance. | L2 | 6M |

OR

- | | | | |
|----|---|----|----|
| 10 | a Derive the expression for Stability Factor S of a Fixed Bias Circuit. | L3 | 6M |
| | b Discuss about Thermal Runaway and Thermal Resistance. | L2 | 6M |

*** END ***