

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

B. TECH II Year I Semester Supplementary Examinations December-2021

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to AGE, CSE & CSIT)

Time: 3 hours

Max. Marks: 60


(Answer all Six Units 6 X 10 = 60 Marks)

PART - A**UNIT-I**


- 1 a Define RMS value, average value, form factor and peak factor. 5M
b Show the form factor of the sine current is 1.11./ Find form factor of the sine current. 5M

OR

- 2 Find the current delivered by the source for the circuit shown in figure. 10M

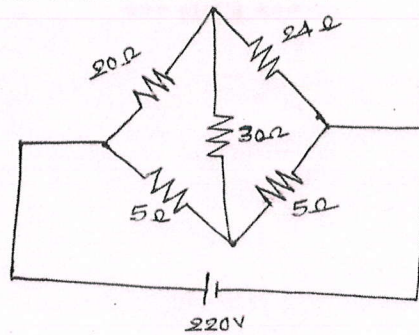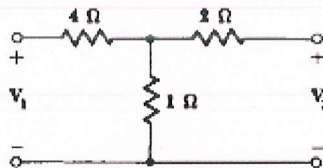**UNIT-II**

- 3 Find the Short circuit parameters for the circuit shown in fig. 10M



OR

- 4 State and prove Reciprocity theorem with an example. 10M

UNIT-III

- 5 a Explain about principle of operation of DC Motors in detail. 5M
b Calculate the value of Torque established by the armature of a 4-pole motor having 774 conductors, 2 paths in parallel, 24 mwb flux per pole when the total armature current is 50A. 5M

OR

- 6 a Explain principle of operation of transformer. 5M
b An ideal transformer has 1000 turns on its primary and 500 turns on its secondary the driving voltage of primary side is 100V and the load resistance is 5 Ω, calculate V2, I1 and I2. 5M

PART - B**UNIT-I**

- 7 Discuss the conduction properties of semiconductors and explain the process of electron hole Pair generation and recombination. 10M

OR

- 8 a Write notes on Diode Specifications and Diode Applications. 6M
b Explain Drift and Diffusion currents in a PN Junction Diode. 4M

UNIT-II

- 9 Draw the circuit diagram for a common base circuit arrangement and plot its input and Output characteristics. Show the different regions of the output characteristics and explain their occurrence. **10M**

OR

- 10 a Describe the constructional features of a Junction Field Effect Transistor. What is the Difference between a P type and N type JFET? Draw the cross sectional view and show the Symbolic representation of each type of the transistor. **5M**
- b Explain in detail the theory of operation of n-channel JFET. **5M**

UNIT-III

- 11 a Mention the types of RC oscillators. Explain RC phase shift oscillator with diagram. **5M**
- b Explain Wein bridge oscillator with diagram. **5M**

OR

- 12 a Discuss the Characteristics of an ideal operational amplifier. **5M**
- b With neat diagram, explain Summing Amplifier. **5M**

***** END *****