

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech III Year I Semester Regular Examinations December-2021**

**POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 Briefly explain about Insulated Gate Bipolar Transistor and its switching characteristics. **L2 12M**

**OR**

- 2 Explain the Resistance firing circuit with the necessary waveforms. **L2 12M**

**UNIT-II**

- 3 Explain the operation of single phase Full wave converter with R load and necessary waveforms. Also derive the output voltage, output current, RMS output voltages. **L2 12M**

**OR**

- 4 a A single phase full converter is made to deliver a constant load current. For zero firing angle, the overlap angle is  $15^\circ$ , calculate the overlap angle when firing angle is i)  $30^\circ$  ii)  $45^\circ$  and iii)  $60^\circ$  **L3 6M**

- b What is the difference between half controlled and fully controlled bridge rectifier. **L2 6M**

**UNIT-III**

- 5 What is a dc chopper? Describe various types of chopper configurations. With appropriate diagram wherever necessary. **L4 12M**

**OR**

- 6 The buck converter has an input voltage of  $E_{dc} = 12V$  the required average output voltage is  $E_o = 5V$  at  $R = 500\Omega$  and the peak to peak output voltage is  $20mV$ , the switching frequency is  $25KHZ$ . If the peak to peak ripple current of inductor is limited to  $0.8A$ , determine (i) The duty cycle (ii) The filter inductance L (iii) The filter Capacitance C. (iv) The critical values of L and C. **L3 12M**

**UNIT-IV**

- 7 Explain the operation of single phase to single phase bridge type step-up cyclo-converter with continuous mode. **L2 12M**

**OR**

- 8 Explain bridge type step-up cycloconverter with RL load for discontinuous conduction mode. **L4 12M**

**UNIT-V**

- 9 Explain the operation of single phase full wave ac voltage controller with R-L load. **L2 12M**

**OR**

- 10 Explain the operation of TRIAC firing circuit. **L2 12M**

\*\*\* END \*\*\*