

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations Feb-2021

SWITCHING THEORY & LOGIC DESIGN

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

1 a Convert the given decimal number 234 to binary, quaternary, octal, hexadecimal and BCD equivalent. 6M

b Simplify the following Boolean expression:

$$F = (A+B)(A'+C)(B+C). \quad 6M$$

OR

2 a Simplify the following Boolean expressions to minimum no. of literals 6M

$$F=(BC'+A'D)(AB'+CD')$$

b State Duality theorem. List Boolean laws and their Duals 6M

UNIT-II

3 a Simplify the following Boolean expressions using K-map 6M

$$F(W,X,Y,Z)= XZ+W'XY'+WXY+W'YZ+WY'Z \text{ Implement using NAND gates.}$$

b Implement the following Boolean function using NOR gates. $Y=(AB'+A'B)(C+D')$. 6M

OR

4 a Minimize the given Boolean function $Y(A,B,C,D) = \Sigma(1,3,5,8,9,11,15)$ using tabulation method and implement using basic gates 6M

b i) Write the advantages of Tabulation method over K-Map method. 6M

ii) Write the given Boolean expression $f = A+B$ in Sum of minterms.

iii) SOP of $F(x, y, z)=\Sigma(2, 3, 6, 7)$.

UNIT-III

5 a Design & implement a 4 bit binary-to-BCD code converter 6M

b Design & implement Full Adder using Two Half adder and OR gate 6M

OR

6 a Implement the following Boolean function using 8:1 multiplexer $F(A,B,C,D) = A'BD'+ACD+B'CD+A'C'D$ 6M

b Implement 2-bit Magnitude Comparator and write down its design procedure. 6M

UNIT-IV

- 7 a Draw the logic symbol, characteristics table and derive characteristics equation of JK flip flop. 6M
- b Implement 6-bit ring counter using suitable shift register. Briefly describe its operation. 6M

OR

- 8 a Draw the circuit of Master Slave JK flip flop using NAND gates and explain its operation. 6M
- b Design T Flip Flop by using JK Flip Flop and draw the timing diagram. 6M

UNIT-V

- 9 a Implement the following Boolean function using PLA 6M
 $F1 = \sum m(0,1,2,3,8,10,12,14)$ $F2 = \sum m(0,1,2,3,4,6,8,10,12,14)$
- b Explain the minimization procedure for determining the set of equivalent state of a specified machine M. 6M

OR

- 10 a Given the 8-bit data word 01011011, generate the 12-bit composite word for the hamming code that corrects and detects single errors . 6M
- b Give the logic implementation of a 32x4 bit ROM using a decoder of a suitable figure. 6M

*** END ***