

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations February-2021

NETWORK ANALYSIS AND SYNTHESIS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Derive the relationship of voltage and current in delta connected load. 6M
 b A balanced star connected load having an impedance $(15+j20) \Omega$ per phase is connected to a three phase 440 V,50Hz supply. Find line currents and phase voltages. Assume RYB phase sequence and also calculate power drawn by the load. 6M

OR


- 2 a A balanced delta connected load of $(4+j3) \Omega$ per phase is connected to a balanced 3 ϕ 400V supply. Find a) active power b) reactive power c) Apparent power. 6M
 b Briefly explain two wattmeter method to measure real power and reactive power: 6M

UNIT-II

- 3 a Derive the transient response of an RL circuit with DC excitation. 8M
 b A series RC circuit consists of resistor of 10 and capacitor of 0.1F has a constant voltage of 20V is applied to the circuit at $t=0$. Obtain the current equation. Determine the voltage across the resistor and the capacitor. 4M


OR

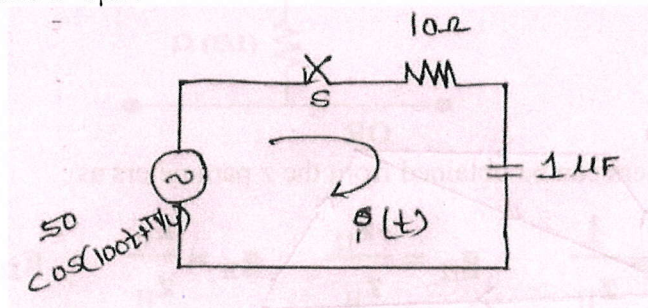- 4 a Derive the transient response of an RL circuit with sinusoidal excitation. 7M
 b In the circuit shown in fig. Determine the complete solution for the current when switch is closed at $t=0$, applied voltage is $V(t)=50\cos(10^2t+\pi/4)$, resistance $R=10\Omega$ and capacitance $c=1\mu F$. 5M




UNIT-III

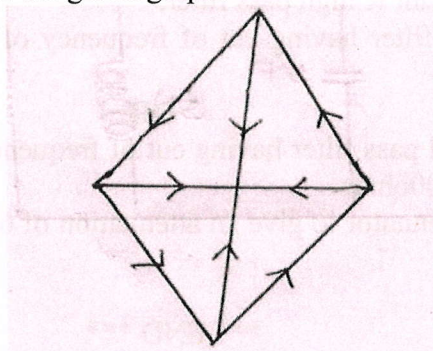- 5 a Find the cut set matrix for the given graph: 6M




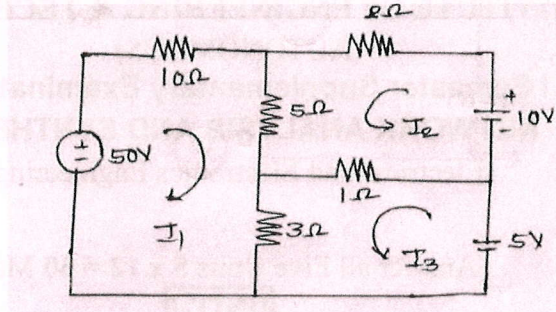b Determine mesh currents for the following network using 6M network topology.




OR

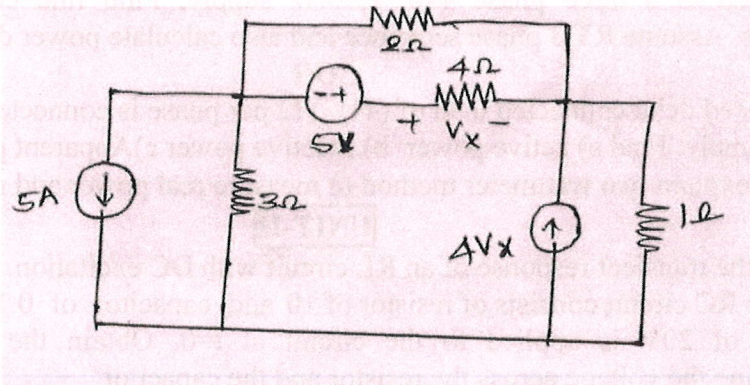- 6 a Define graph, oriented graph, tie set and cutset 4M
 b Draw the dual network: 8M



UNIT-IV

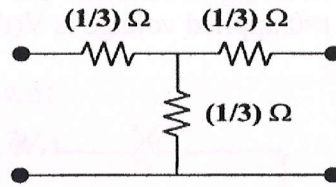- 7 a Derive Z parameters in term of transmission parameters: 6M
 b Determine y parameters: 6M



OR

- 8 a Prove the g parameters can be obtained from the z parameters as 6M

$$g_{11} = \frac{1}{z_{11}} \quad g_{12} = \frac{-z_{12}}{z_{11}} \quad g_{21} = \frac{z_{21}}{z_{11}} \quad g_{22} = \frac{\Delta_z}{z_{11}}$$

- b Derive the condition for reciprocity in h-parameters: 6M

UNIT-V

- 9 a Explain about constant K high pass filter. 6M
 b Design a low pass filter having cut of frequency of 2KHz with load resistance of 500ohms. 6M

OR

- 10 a Design K-type band pass filter having cut of frequency of 2KHz & 10KHz and with load resistance of 600ohms. 6M
 b Design a T- pad attenuator to give an attenuation of 60dB and to work in line of 500 ohms impedance. 6M

*** END ***