

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations Feb-2021

ELECTRONIC DEVICES

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- |   |   |   |    |
|---|---|---|----|
| 1 | a | Define Breakdown Voltage of a PN junction diode.                          | 2M |
|   | b | List applications of Zener Diode.   | 2M |
|   | c | In a BJT, if a transistor has $\alpha = 0.97$ , find the value of $\beta$ | 2M |
|   | d | Draw the simplified hybrid model for CC amplifier.                        | 2M |
|   | e | Define Pinch off Voltage.   | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |   |   |   |    |
|---|---|---|----|
| 2 | a | Draw and explain forward and reverse biasing of a PN Junction diode with V-I Characteristics. | 5M |
|   | b | Derive the Diode Current Equation.  | 5M |

**OR**

- |   |   |  |    |
|---|---|--|----|
| 3 | a | Discuss the importance of Diode Clipper and explain the Positive and Negative Diode clippers.  | 5M |
|   | b | Determine the value of forward current in the case of a PN junction diode, with $I_0 = 10\mu\text{A}$ , $V_f = 0.8\text{V}$ at $T = 3000\text{K}$ . Assume Silicon Diode | 5M |

**UNIT-II**

- |   |   |   |    |
|---|---|---|----|
| 4 | a | Derive the expressions for Ripple Factor and Efficiency of Half Wave Rectifier. | 5M |
|   | b | Draw and describe VI characteristics of Tunnel Diode.                           | 5M |

**OR**

- |   |   |  |    |
|---|---|--|----|
| 5 | a | Draw and explain Bridge Rectifier.                       | 5M |
|   | b | Explain the construction and applications of Solar Cell. | 5M |

**UNIT-III**

- |   |   |  |    |
|---|---|--|----|
| 6 | a | Define Transistor Biasing and explain the need for Biasing?                                  | 5M |
|   | b | Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. | 5M |

**OR**

- |   |   |   |    |
|---|---|---|----|
| 7 | a | Discuss the Input and Output characteristics of a BJT in CE Configuration. Indicate the regions of operations in the output characteristics.  | 6M |
|   | b | If the base current in a transistor is $20\mu\text{A}$ when the emitter current is $6.4\text{mA}$ , what are the values of $\alpha$ and $\beta$ ? also calculate the collector current. | 4M |

**UNIT-IV**

- |   |   |   |    |
|---|---|---|----|
| 8 | a | Determine the parameters $A_i$ , $R_i$ , $A_v$ and $R_0$ of Emitter Follower using simplified hybrid model analysis.  | 6M |
|   | b | A voltage source of internal resistance $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$ . The CE h parameters are $h_{fe} = 60$ , $h_{ie} = 1200\Omega$ , $h_{oe} = 25\mu\text{A/V}$ and $h_{re} = 2 \times 10^{-4}$ . Compute $A_i$ , $R_i$ , $A_v$ and $R_0$ using approximate analysis. | 4M |

OR


- 9 a Draw the circuit diagram of a single stage RC coupled Amplifier and discuss the steps used for designing it. 5M
- b Determine Voltage Gain, Current Gain, Input resistance and Output resistance for a CE amplifier using NPN transistor with  $h_{ie} = 1200\Omega$ ,  $h_{re} = 0$ ,  $h_{fe} = 36$  and  $h_{oe} = 2 \times 10^{-6}$  mhos,  $R_L = 2.5k\Omega$  and  $R_S = 500\Omega$  (neglect the effect of biasing circuit). 5M

## UNIT-V

- 10 a Define the JFET Volt-Ampere Characteristics and determine FET parameters. 5M
- b Compare the performance of BJT with FET. 5M

OR

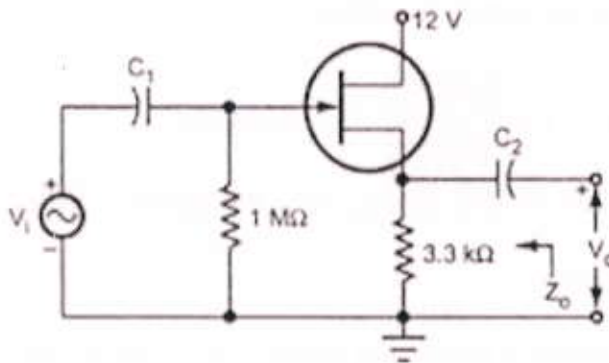- 11 a For Common Drain Amplifier as shown in the Figure,  $g_m = 2.5mS$ ,  $r_d = 25K\Omega$ . Calculate Input impedance, Output impedance and Voltage gain. 5M



- b List and explain the steps involved in the manufacturing process of monolithic ICs. 5M

\*\*\*END\*\*\*