

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations February-2022

BASIC ELECTRICAL ENGINEERING

(Common to ECE, CSE & CSIT)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions **5 x 2 = 10** Marks)


- | | | | |
|----------|----------|---|-----------|
| 1 | a | What are the Limitations of Superposition Theorem? | 2M |
| | b | Define Form Factor and Peak Factor. | 2M |
| | c | What happens when transformer is given DC supply? | 2M |
| | d | Why an induction motor is called a rotating transformer? Justify. | 2M |
| | e | Define Fuse and Circuit Breaker. | 2M |

PART-B

(Answer all Five Units **5 x 10 = 50** Marks)


UNIT-I

- | | | | |
|----------|----------|---|-----------|
| 2 | a | Derive the time response of RC circuit. | 5M |
| | b | Determine the current in branch A-B by using KVL. | 5M |

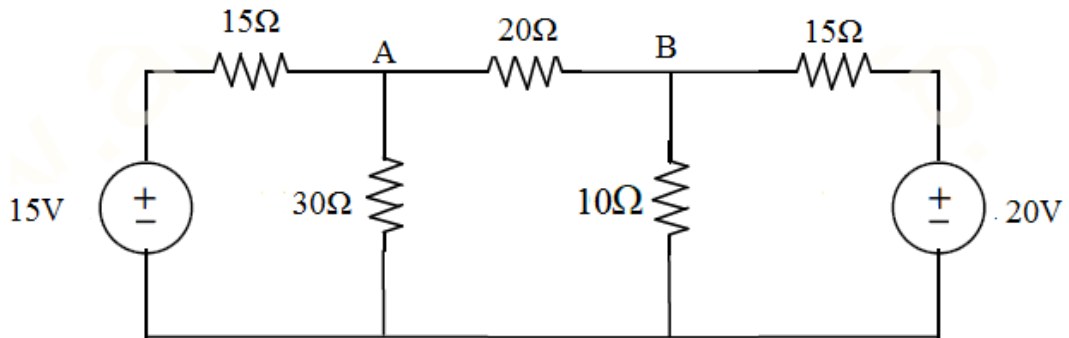

OR

- | | | | |
|----------|----------|---|-----------|
| 3 | a | State and Explain Thevenin's Theorem. | 4M |
| | b | Find load current by using Thevenin's theorem for the following circuit where $R_L=3\Omega$ | 6M |

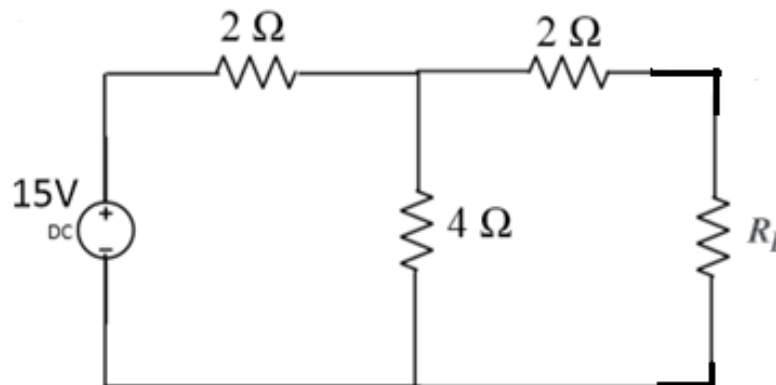

UNIT-II

- | | | | |
|----------|----------|---|-----------|
| 4 | a | Derive an expression for RMS values of sine wave form. | 6M |
| | b | An alternating current is expressed as $I = 14.14 \sin 314t$. Determine
(i). Maximum current (ii). RMS Current (iii). Frequency (iv). Instantaneous current
when $t = 0.02\text{msec}$ | 4M |

OR

- 5 a Explain resonance for series RLC circuit and derive the equation for resonant frequency? **5M**
b A series RLC circuit of $R=50$ ohms, $L= j25$ ohms. Determine the value of capacitive reactance and impedance at resonance. **5M**

UNIT-III

- 6 a Explain the various losses in a transformer. **5M**
b The efficiency of a 200 KVA, 1- Φ transformer is 98% when operating at full-load, 0.8 p.f lagging, the iron loss in the transformer is 400 W. Calculate: (i) Full load copper loss (ii) Half load copper loss. **5M**

OR

- 7 What are three phase transformer connections and explain it? **10M**

UNIT-IV

- 8 Explain the various method of speed control of separately excited DC motor. **10M**

OR

- 9 Explain the construction details and working principle of Alternator. **10M**

UNIT-V

- 10 Explain in detail different methods used for improvement of power factor. **10M**

OR

- 11 a How many types of batteries are there? **5M**
b Explain the characteristics of batteries? **5M**

END