

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech I Year II Semester Supplementary Examinations February-2022**

**BASIC ELECTRICAL ENGINEERING**  
(Electronics and Communication Engineering)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

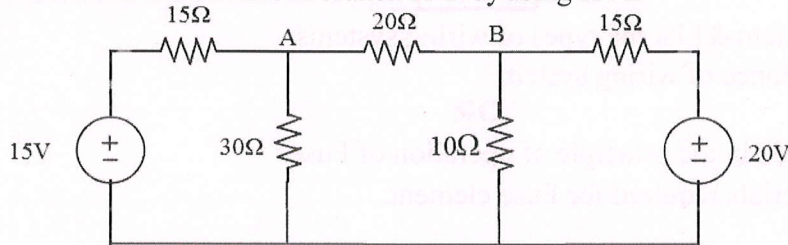
**UNIT-I**

- 1 a State and explain Kirchoff's laws? 6M  
b Determine the current in branch A-B by using KVL 6M




OR

- 2 a State and Prove Maximum Power Transfer Theorem. 6M  
b Find load current by using Thevenin's theorem for the following circuit when  $R_L=3\Omega$ . 6M

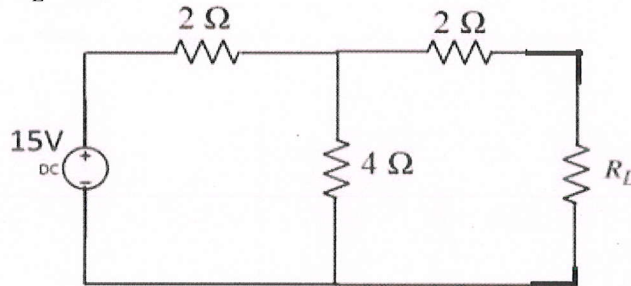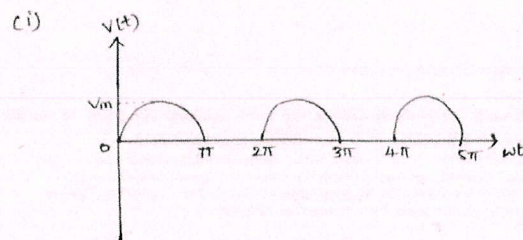**UNIT-II**

- 3 a Derive an expression for the current and impedance for a series RL and RC circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams. 8M  
b Define Admittance and impedance. 4M
- OR
- 4 a Derive the voltage and current relations in three phase balanced circuits for star connection. 7M  
b Find the rms value for the following waveform. 5M



**UNIT-III**

- 5 List the various types of D.C. Generators and Explain in detail with neat sketch. 12M
- OR**
- 6 a Derive the EMF equation of a D.C generator. 5M  
b Explain Open Circuit Characteristics of D.C. generator with neat sketch. 7M

**UNIT-IV**

- 7 a Explain the Working principle of single phase transformer. 6M  
b Compare Core type & Shell type transformer. 6M
- OR**
- 8 a Explain the Principle and Working of 3- $\emptyset$  Alternator. 8M  
b Distinguish between Salient and Non-Salient Pole rotors used in Alternator. 4M

**UNIT-V**

- 9 a Define Wiring system & List the types of wiring systems. 8M  
b What is the importance of wiring system? 4M
- OR**
- 10 a What is Fuse & explain the principle of operation of Fuse. 6M  
b What are the Materials required for Fuse element. 6M

\*\*\* END \*\*\*