

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations February-2022

ANALOG CIRCUITS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | |
|---|---|---|----|
| 1 | a | Why h-parameter model is not suitable for high frequencies? | 2M |
| | b | What is positive feedback and negative feedback? | 2M |
| | c | Classify different types of power amplifiers. | 2M |
| | d | What is operational amplifier? | 2M |
| | e | Classify active filters. | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | |
|---|---|---|----|
| 2 | a | Derive the expression for Hybrid- π capacitance of CE transistor at high frequency. | 5M |
| | b | Derive the expression for the hybrid- π parameters $r_{bb'}$ and g_{ce} | 5M |

OR

- | | | | |
|---|---|---|----|
| 3 | a | Describe the variation of hybrid- π parameters upon collector current, VCE and Temperature. | 5M |
| | b | If $I_c = 1\text{mA}$ and $V_{CE} = 10\text{V}$, a certain transistor data shows $C_c = C_{b'c} = 3\text{pF}$, $h_{fe} = 200$ and $\omega_T = -500\text{ M rad/sec}$. Calculate g_m , $r_{b'e}$, $C_e = C_{b'e}$ and ω_β | 5M |

UNIT-II

- | | | | |
|---|---|---|----|
| 4 | a | Explain the concept of negative feedback with the help of a neat block diagram. | 5M |
| | b | Discuss voltage amplifier and current amplifier with neat diagram. | 5M |

OR

- | | | | |
|---|---|---|----|
| 5 | a | Derive the expressions of input and output resistances for Voltage Series FBA. | 5M |
| | b | A voltage series negative feedback amplifier has a voltage gain without feedback of $A = 500$, input resistance $R_i = 3\text{k}\Omega$, output resistance $R_o = 20\text{k}\Omega$ and feedback ratio $\beta = 0.01$. Calculate the voltage gain A_f , input resistance R_{if} , and output resistance R_{of} of the amplifier with feedback. | 5M |

UNIT-III

- | | | | |
|---|---|--|----|
| 6 | a | Discuss on crossover distortion in class B power amplifier. | 5M |
| | b | Describe the operation of a single tuned capacitive coupled amplifier with diagram and derive the expression for its central frequency and Quality factor. | 5M |

OR

- | | | | |
|---|---|---|----|
| 7 | a | Discuss Double Tuned Amplifier with neat diagram. | 6M |
| | b | Derive the expression for Double Tuned Amplifier bandwidth. | 4M |

UNIT-IV

- | | | | |
|---|--|---|-----|
| 8 | | Draw an inverting amplifier using an op amp and derive the expression for its closed loop voltage gain. | 10M |
|---|--|---|-----|

OR

- | | | | |
|---|---|--|----|
| 9 | a | Draw the circuit diagram of a Differential Amplifier and derive the expression for its output voltage. Write about difference and common mode gains. | 5M |
| | b | Explain the block diagram of an internal circuit of an operational amplifier. | 5M |

UNIT-V

- 10 a Draw a general Sallen-Key Filter and determine its transfer function and from general Sallen Key Filter obtain the transfer function of second order active low pass filter. **5M**
- b Classify Band pass filter. Mention the important parameters of a band pass filter. **5M**
Draw Second order narrow band pass filter .
- OR**
- 11 a Design a high pass filter with cutoff frequency of 1 KHz and a pass band gain of 2. **5M**
- b What is a notch filter? How do we get a notch filter from a band pass filter? Draw the circuit schematic of a second order notch filter and obtain its transfer function. **5M**

END