

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Supplementary Examinations February-2022**

**SWITCHING THEORY AND LOGIC DESIGN**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 Express the function  $Y=A+B'C$  in L3 12M  
(i) Canonical SOP form (ii) Canonical POS form

**OR**

- 2 A receiver with even parity hamming code is received the data as 1110110. L3 12M  
Determine the correct code.

**UNIT-II**

- 3 Minimize the given Boolean function L2 12M  
 $F(A,B,C,D) = \sum m(2,3,5,7,8,10,12,13)$  using tabulation method.

**OR**

- 4 Simplify the following Boolean expressions using K-map. L3 12M  
 $F(A, B, C, D) = \pi M(0,2,3,8,9,12,13,15)$

**UNIT-III**

- 5 What is Encoder? Design the circuit for Octal to Binary encoder with truth table L1 12M

**OR**

- 6 What is Demultiplexer? Design 1:8 Demultiplexer using 1:4 Demultiplexers. L1 12M

**UNIT-IV**

- 7 Design and implement 3-bit ripple counter using J-K flip flop. Draw the state L3 12M  
diagram, logic diagram and timing diagram for the same.

**OR**

- 8 a Draw the logic diagram for D Flip Flop by using SR Flip Flop Explain the L1 6M  
operation with truth table.  
b Write the differences between combinational and sequential circuits L2 6M

**UNIT-V**

- 9 Implement the following Boolean function using PAL. L3 12M  
(i)  $W(A,B,C,D) = \sum m(0,2,6,7,8,9,12,13)$   
(ii)  $X(A,B,C,D) = \sum m(0,2,6,7,8,9,12,13,14)$   
(iii)  $Y(A,B,C,D) = \sum m(2,3,8,9,10,12,13)$   
(iv)  $Z(A,B,C,D) = \sum m(1,3,4,6,9,12,14)$

**OR**

- 10 a What is FSM? Give the applications of FSM. L3 6M  
b Explain about Memory decoding. L3 6M

\*\*\* END \*\*\*