

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations February-2022

ELECTRONIC CIRCUIT ANALYSIS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

- 1 a With the help of necessary circuit diagrams and approximations, deduce the expression for CE short circuit current gain. L4 8M
- b A BJT has $g_m = 38$ mhos, $r_{be} = 5.9k\Omega$, $h_{ie} = 6k\Omega$, $r_{bb} = 100\Omega$, $C_{bc} = 12pF$, $C_{be} = 63pF$ and $h_{fe} = 224$ at 1 KHz. Calculate α , β cutoff frequencies and f_T L3 4M

OR

- 2 a Explain the effect of Cascading on bandwidth in multistage amplifiers. L2 6M
- b With neat diagram, explain Cascode amplifier and deduce the expressions for voltage gain. L4 6M

UNIT-II

- 3 a Explain Feedback amplifier topologies with necessary diagram. L2 6M
- b Show that bandwidth of an amplifier can be extended by using negative feedback amplifier. L2 6M

OR

- 4 a Explain the effect of negative feedback on input resistance for Current shunt and Voltage shunt Feedback amplifier. L2 6M
- b Compare various types of feedback amplifiers. L4 6M

UNIT-III

- 5 a Establish the condition for oscillation with suitable diagram L3 6M
- b Determine the frequency of oscillations when a RC phase shift oscillator has $R=100$ k Ω , $C=0.01\mu F$ and $RC = 2.2$ K Ω . Also find the minimum current gain needed for this purpose. L3 6M

OR

- 6 a Explain the working principle of Wein-bridge oscillator using BJT and deduce the expression for frequency of oscillations. L4 7M
- b A Colpitts oscillator is designed with $C_1 = 150$ pF and $C_2 = 6500$ pF. The inductance is variable. Determine the range of inductance values, if the frequency of oscillation is to vary between 950 KHz to 2050 KHz. L3 5M

UNIT-IV

- 7 a Discuss Complementary Symmetry Class B Push Pull Power Amplifier with neat diagram and determine its efficiency. **L3 6M**
- b Write notes on crossover distortion in class B power amplifier. **L3 6M**

OR


- 8 a With circuit diagram, describe the stagger tuning operation. Sketch necessary graph. **L3 7M**
- b The bandwidth of a single tuned amplifier is 20 kHz. Determine the bandwidth if three such stages are cascaded. Also calculate the bandwidth for four stages. **L3 5M**

UNIT-V

- 9 a Deduce the expression for time period, T in Astablemultivibrator. **L4 8M**
- b List the applications of Astable and Monostable multivibrators. **L1 4M**

OR

- 10 a Why the triggering is needed for multivibrators? Explain a triggering method for monostable multivibrator. **L2 6M**
- b Calculate the stable state currents and voltages for the bistable multivibrator having $V_{CC} = 12\text{ V}$, $V_{BB} = -12\text{ V}$, $R_{C1} = R_{C2} = 2.2\text{ k}\Omega$, $R_1 = R_2 = 15\text{ k}\Omega$, $R_3 = R_4 = 100\text{ k}\Omega$, $C_1 = C_2 = 0.1\text{ }\mu\text{F}$. Assume that a transistor having a minimum h_{fe} of 20 is used. **L4 6M**

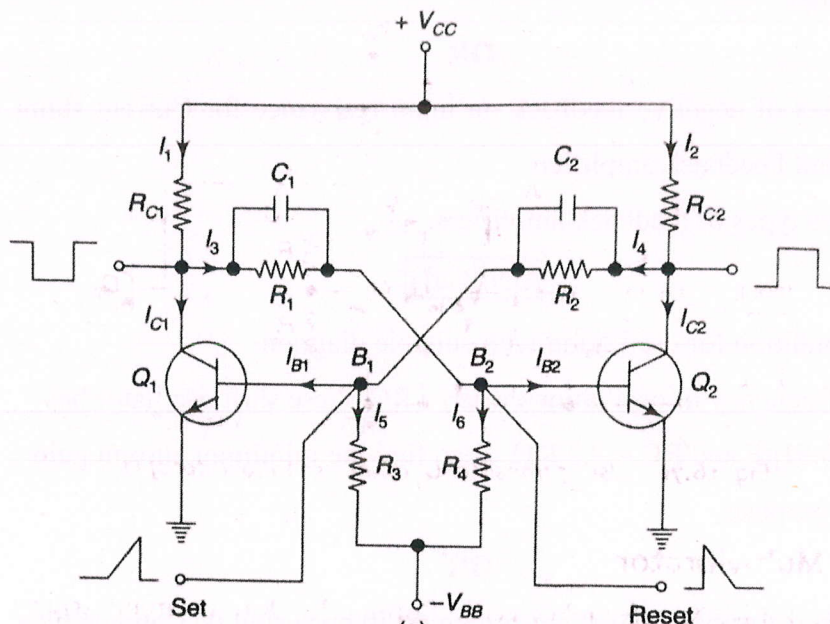

*** END ***