

Q.P. Code: 16EE201

R16

Reg. No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations Dec 2019

ELECTRICAL CIRCUITS
(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks:60


(Answer all Five Units 5 X 12 = 60 Marks)

UNIT-I


- 1 Derive the expression for Delta connected resistances in terms of Star connected resistances? 12M

OR

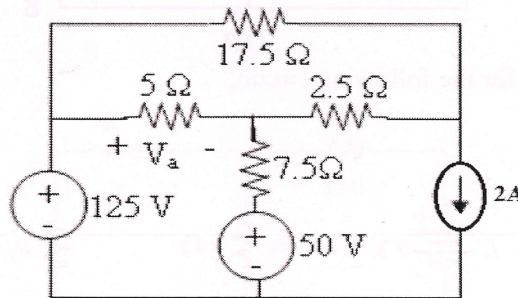- 2 a Find the value of V_a for the following circuit using KVL.



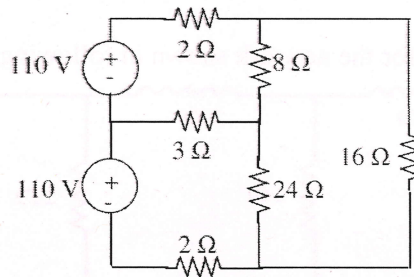- b Using nodal analysis find all branch currents for the following circuit.



UNIT-II

- 3 Determine the average value, RMS value, Form factor and peak factor of a pure sinusoidal waveform? 12M

OR

- 4 A $1K\Omega$ resistor is connected in series with an inductance of 50mH across a 230V, 50HZ AC Supply. Find (i) Inductive reactance (ii) Impedance (iii) Current (iv) Phase angle (v) Voltage drop across resistance (vi) Voltage drop across Inductance. 12M

UNIT-III

- 5 Obtain the expression for resonant frequency, bandwidth and Q-factor for Series R-L-C circuit. 12M

OR

- 6 A series RLC circuit has $R=10\Omega$, $L=0.5H$ and $C=40\mu F$. The applied voltage is 100V. Find (i) Resonant frequency & Quality factor of a coil (ii) Bandwidth (iii) Upper and lower Half power frequencies (iv) Current at resonance & current at half power points (v) Voltage across inductance & voltage across capacitance at resonance. 12M

UNIT-IV

- 7 A coil of 100 turns is wound uniformly over a insulator ring with a mean circumference of 2m and a uniform sectional area of $0.025cm^2$. If the coil is carrying a current of 2A. Calculate (i) The mmf of the circuit (ii) magnetic field intensity (iii) flux density (d) total flux. 12M


OR

Q.P. Code: 16EE201

8 Explain Self Inductance, Mutual Inductance and Co-efficient of coupling in detail? Give the Relation between L1, L2, K & M? 12M


UNIT-V

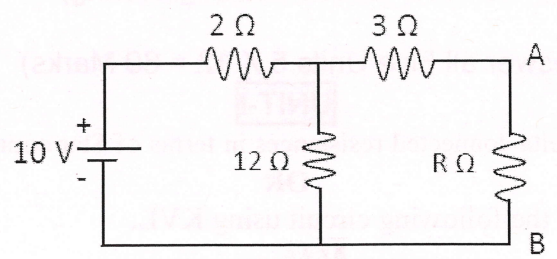9 a State and explain super position theorem. 6M
b Find the maximum power delivered to the load by using maximum power transfer theorem for the following circuit. 6M




OR

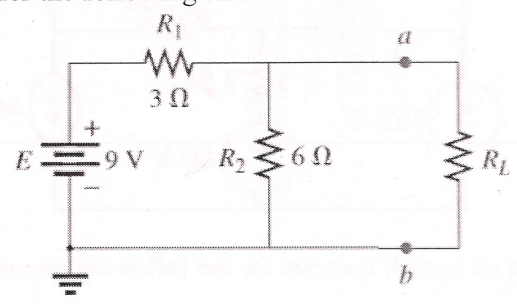10 a Find Norton's equivalent for the following circuit. 6M



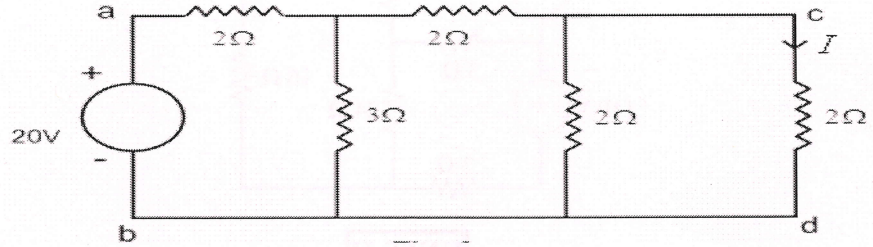b Verify the reciprocity theorem for the network shown in following circuit. 6M



*** END ***