

Reg. No. [] [] [] [] [] [] [] [] [] []

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR (AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations Dec 2019

NETWORK ANALYSIS

(Electronics & Communication Engineering)


Time: 3 hours

Max. Marks:60

(Answer all Five Units 5 X 12 = 60 Marks)


UNIT-I

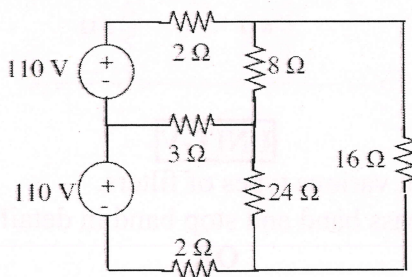- 1 a State and explain Kirchoff's laws? 4M
- b Using nodal analysis find all branch currents for the following circuit 8M



OR

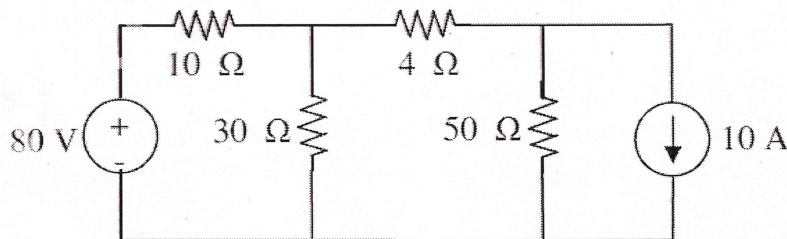- 2 a What is the condition for maximum power transfer to the load? 4M
- b Verify Superposition theorem for 4Ω resistor for the following circuit. 8M



UNIT-II

- 3 a Explain the phasor relation for parallel RLC circuit. 6M
- b A parallel RLC circuit is supplied with a voltage source of 230 V, 50Hz. Determine circuit current and power factor if $R=40\Omega$, $L=0.2H$ and $C=50\mu F$. 6M

OR

- 4 a Explain the characteristics of sinusoids. 4M
- b The impedances of parallel circuit are $Z_1 = (4+j6)$ ohms and $Z_2 = (12-j8)$ ohms. If the applied voltage is 220V, find (i) current and power factor of each branch (ii) overall current (iii) power consumed by each impedance. Draw the phasor diagram. 8M

UNIT-III


- 5 Obtain the expression for resonant frequency, bandwidth and Q-factor for Series R-L-C circuit. 12M

OR

- 6 a Explain about dot convention in mutually coupled circuits. 6M
- b Define and explain self and mutual inductance. 6M

UNIT-IV

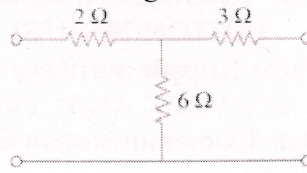
7 a Find the ABCD parameters for the following circuit. 6M



b Express Y parameters in terms of h parameters. 6M

OR

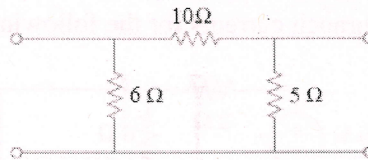8 Find the ABCD and h - parameters for the following circuit. 12M



UNIT-V

9 a What is a filter? Explain about various types of filters. 4M

b Explain the classification of pass band and stop band in detail. 8M

OR

10 What is high pass filter? Explain the general configuration and parameters of a constant-K high pass filter. 12M

***** END *****