

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)
B.Tech I Year II Semester Supplementary Examinations December 2018
NETWORK ANALYSIS
(ECE)


Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 X 12 = 60 Marks)


UNIT-I

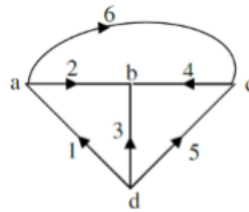- 1 a. Define the following terms (i) Branch (ii) Sub graph (iii) Node (iii) Tree 4M
b. For the graph shown below find incidence and cut set matrices. 8M



OR

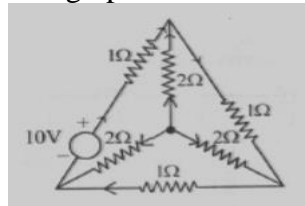- 2 a. Define and state the properties of incidence matrix. 4M
b. For the network shown below draw the graph and find incidence and tie – set matrices 8M



UNIT-II

- 3 a. Explain the characteristics of sinusoids. 4M
b. A resistor of 150Ω , inductance of 200mH and a capacitance of $10\mu\text{F}$ are connected in series across 500V , 150Hz supply. Determine the following 8M
(i) Impedance (ii) current flowing through the circuit (iii) power factor
(iv) voltage across R,L &C (v) power in watts

OR

- 4 a. Explain the complete response of source free series RLC Circuits. 6M
b. Explain about Natural & Forced Response of RLC Circuits. 6M

UNIT-III


- 5 a. Obtain the expression for resonant frequency, bandwidth and Q-factor of parallel RLC circuit. 6M
b. Obtain the expression for resonant frequency, bandwidth and Q-factor of Series RLC circuit. 6M

OR

- 6 a. Explain about dot convention in mutually coupled circuits. 4M
b. Explain about linear transformer and ideal transformer. 8 M

UNIT-IV

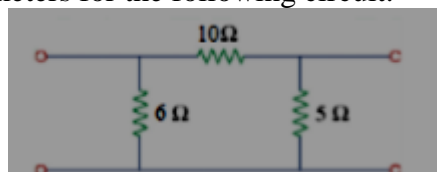- 7 a. Express Z parameters in terms of ABCD parameters. 4M
b. Find the ABCD and h - parameters for the following circuit. 8M



OR

- 8 a. Explain about the state variables and state variables of circuits. 10M
b. What are the advantages of state variable analysis? 2M

UNIT-V

- 9 Design a constant K high pass filter and explain its design procedure in detail. 12M

OR

- 10 What is high pass filter? Explain the general configuration and parameters of a constant -K high pass filter. 12M

***** END *****