

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)  
B.TECH I Year II Semester (R16) Supplementary Examinations Dec 2017  
NETWORK ANALYSIS  
(ECE)**


Time: 3 hours

Max. Marks:60

(Answer all Five Units 5 X 12 = 60 Marks)

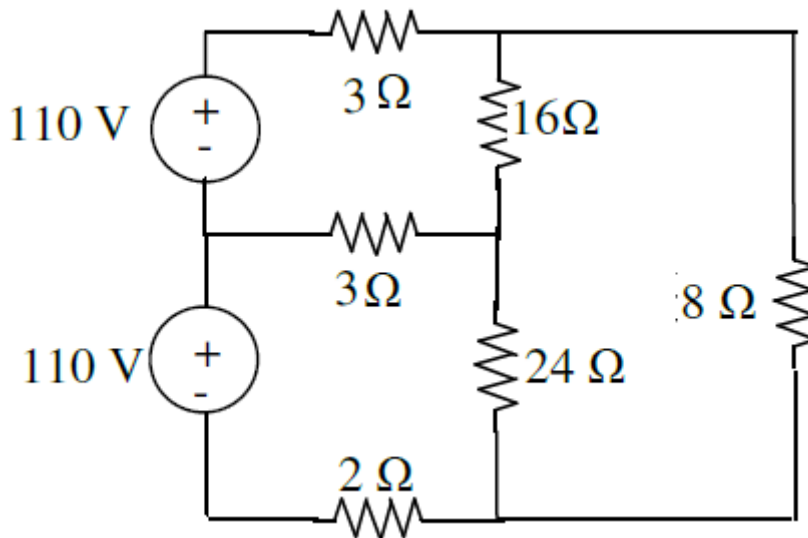**UNIT-I**

- 1 a State and explain Kirchhoff's laws? 4M  
 b Using nodal analysis find all branch currents for the following circuit



8M

**OR**

- 2 a Define the following terms 4M  
 i. Branch ii. Sub graph iii. Node iv. Tree  
 b State and explain Norton's theorem? 8M

**UNIT-II**

- 3 a Explain the phasor relation for R,L,C elements. 6M  
 b The impedances of parallel circuit are  $Z_1 = (6+j8)$  ohms and  $Z_2 = (8-j6)$  ohms. If the applied voltage is 120V, find (i) current and power factor of each branch (ii) overall current (iii) power consumed by each impedance. Draw the phasor diagram. 6M

**OR**

- 4 a Explain the complete response of source free parallel RLC Circuits. 6M  
 b Deduce the transient response source free series RL circuit 6M

**UNIT-III**

5 Obtain the expression for resonant frequency, bandwidth and Q-factor for parallel R-L-C circuit. 12M

**OR**

6 Write the comparison between series resonance and parallel resonance? 12M

**UNIT-IV**

7 Explain about the state variables and state variables of circuits. 12M

**OR**

8 Explain about proper and improper behavior of the circuits. 12M

**UNIT-V**

9 Explain the design procedure for a constant K low pass filter and its characteristics 12M

**OR**

10 a What is a filter? Explain about various types of filters 6M

b What is a constant K low pass filter, derive its characteristics impedance 6M

**\*\*\* END \*\*\***