

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Regular Examinations May 2019
ELECTRICAL CIRCUITS-I

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions **5 x 2 = 10** Marks)


- | | | | |
|----------|----------|---|----|
| 1 | a | State Ohm's law and write the limitations of Ohm's law. | 2M |
| | b | Define peak factor. | 2M |
| | c | State superposition theorem. | 2M |
| | d | Define Quality factor. | 2M |
| | e | Write the Faraday's laws of electromagnetic induction. | 2M |

PART-B

(Answer all Five Units **5 x 10 = 50** Marks)

UNIT-I

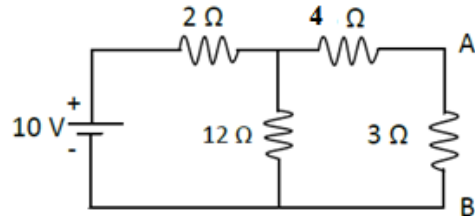
- 2 a** Determine the current in the 3Ω resistor in the network shown in figure.



- b** What are the types of sources? Explain them with suitable diagrams and characteristics.


OR

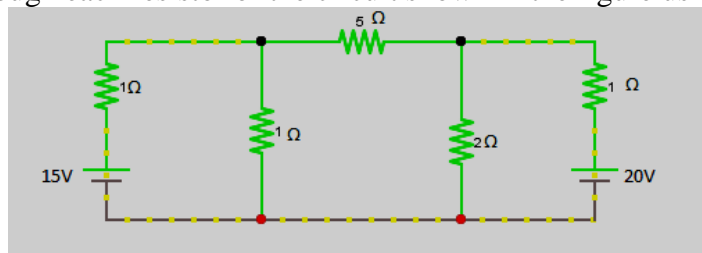- 3 a** Derive an expression for total resistance when three resistances R_1 , R_2 & R_3 are connected in series.
- b** Find the current through each resistor of the circuit shown in the figure using nodal analysis.



UNIT-II

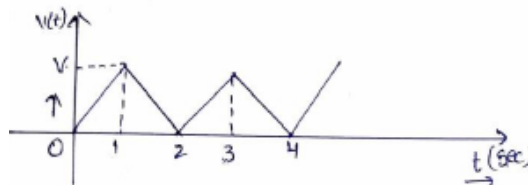
- 4 a** Find the form factor for the following wave form shown in figure.



- b** A pure inductive coil allows a current of 10A to flow from a 230V, 50Hz Ac supply. Find (a) Inductive Reactance (b) Inductance of the coil (c) Power absorbed (d) sinusoidal equations for voltage and current.


OR

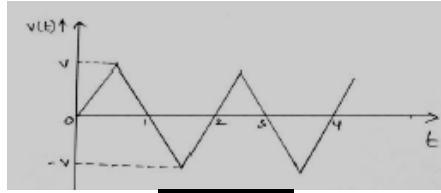- 5 a A Capacitor of $2\mu\text{F}$ is connected across an AC voltage of $V=170 \sin(400t)$. Determine (a) Capacitive Reactance (b) Sinusoidal expression for current (c) Maximum current. 5M
 b Find the form factor for the following waveform shown in figure. 5M



UNIT-III

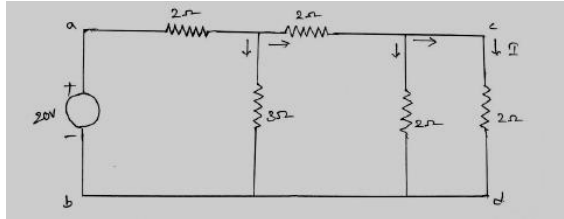
- 6 a Verify reciprocity theorem for the network shown in figure.



- b Derive the condition for the maximum power to be transferred from the source to the load. 5M

OR

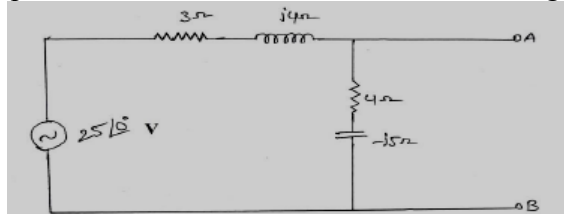- 7 a Determine the Norton's equivalent circuit for the circuit shown in figure.



- b State and explain Millman's theorem. 5M

UNIT-IV

- 8 a In a parallel resonance circuit (Tank circuit) $R=1\Omega$, $L=1 \text{ mH}$ and $C=20\mu\text{F}$, Find the Resonant Frequency, Dynamic impedance and bandwidth. 5M
 b Draw the locus diagram of a series RL circuit. 5M

OR

- 9 a Obtain the expression for resonant frequency, bandwidth and Q-factor for parallel R-L-C circuit. 5M
 b Compare series resonance and parallel resonance. 5M

UNIT-V

- 10 a Compare electric and magnetic circuits and explain the analogy between the electric and magnetic circuits? 5M
 b Derive the expression for equivalent inductance when the coupled inductors are connected in parallel aiding and parallel resonance? 5M

OR

- 11 a Explain Self-inductance, Mutual inductance and Co-efficient of coupling in detail. Give the relation between L_1 , L_2 , K & M . 5M
 b A coil of 100 turns is wound uniformly over a insulator ring with a mean circumference of 1m and a uniform sectional area of 0.025cm^2 . If the coil is carrying a current of 1A. Calculate a) the mmf of the circuit (b) magnetic field intensity (c) flux density (d) total flux 5M

END