

Reg. No. 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY::PUTTUR  
(AUTONOMOUS)**

**M.Tech I year II Semester Regular Examinations June 2019  
DIGITAL CONTROL OF POWER ELECTRONIC AND DRIVE SYSTEMS  
(Power Electronics)**

Time: 3 hours

Max. Marks:60

(Answer all Five Units 5×12=60 Marks)

**UNIT I**

- 1 Explain the application of numerical methods to solve transients in D.C. switched R-C. 12M  
**OR**  
2 Explain the application of numerical methods to solve transients in D.C. switched R-L. 12M

**UNIT II**

- 3 a Discuss the working of diode with R load with AC supply. 6M  
b Discuss the working of diode with R-L load with AC supply. 6M  
**OR**  
4 Write about the modeling of SCR and TRIAC in simulation. 12M

**UNIT III**

- 5 a Explain the electrical machine modeling of DC machine. 6M  
b Give the simulation diagram of basic electric drives. 6M  
**OR**  
6 Explain the State space modeling and simulation of linear systems. 12M

**UNIT IV**

- 7 a Explain the Simulation of single phase uncontrolled rectifiers. 6M  
b Explain the Simulation of single phase controlled (SCR) rectifiers. 6M  
**OR**  
8 What are the power factor correction schemes and explain with neat figures? 12M

**UNIT V**

- 9 Explain in detail the Simulation of thyristor choppers with voltage commutation schemes. 12M  
**OR**  
10 Explain Pulse-width modulation methods for voltage control and Waveform control. 12M

**\*\*\*END\*\*\***