

Reg. No.

--	--	--	--	--	--	--	--	--	--

Q.P. Code:16EE4302

R16

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)
M.Tech I Year I Semester (R16) Supplementary Examinations MAY/June 2017
ANALYSIS OF POWER ELECTRONIC CONVERTERS
(Power Electronics)
(For Students admitted in 2016 only)

Time: 3 hours

Max. Marks:60

(Answer all Five Units 5 X 12 =60 Marks)

UNIT-I

- 1 a. Write short notes on effect of source and load inductance of AC voltage controllers (6M)
- b. Derive the expression for output voltage and output current of AC voltage controller with RL load (6M)

OR

- 2 a. Explain the operation of synchronous tap changer with circuit diagram and necessary waveforms and its applications (6M)
- b. Finding the performance parameters of a 3- Φ delta connected controller has R-load of $R=10\Omega$ and a Line to Line input voltage of 208V at 60HZ, if the delay angle $\alpha=2\pi/3$ Determine (6M)
- a) RMS output phase voltage b) Expressions for the instantaneous currents
c) RMS output phase current d) Input power factor e) RMS thyristor current

UNIT-II

- 3 a. List out the applications of cyclo converters (4M)
- b. Explain the working operation of 1ϕ to 1ϕ midpoint cyclo converter with neat circuit diagram and necessary wave forms? (8M)

OR

- 4 a. What are the applications of single phase converters? (4M)
- b. A single phase converter has RL load of $R=0.5\Omega$, $L=6.5$ mH, the input voltage of 120v at 60 hz. Determine the load current at $\alpha = 60^\circ$ (8M)

UNIT-III

- 5 a. List out the advantages of 3- Φ converters over 1- Φ converters (6M)
- b. Explain the operation of 3- Φ fully controlled converter with neat circuit diagram and wave forms. (6M)

OR

- 6 a. Write a short notes on Buck Boost Regulator b) cuk regulator (6M)
- b. briefly discuss about a) multi output Boost converter b) Application of DC – DC converter (6M)

UNIT-IV

- 7 a. Discuss the following performance parameters of 1- ϕ inverter (4M)
a) Harmonic factor b) Total harmonic distortion
- b. Explain the working operation of 1- ϕ bridge Inverter with circuit diagram and wave forms (6M)

OR

- 8 a. Explain the following advanced modulation techniques (6M)
a) Trapezoidal b) Stair case
- b. Discuss about a) Stepped harmonic Injection b) Delta modulation (6M)

UNIT-V

- 9 A 3- ϕ inverter has a star connected load of $R=5\Omega$ and $L=20\text{mH}$. The inverter frequency of $f_0=60\text{hz}$ and a dc input voltage of $V_s=220\text{V}$ determine (12M)
a) RMS line voltage b) RMS phase voltage c) THD d) HF

OR

- 10 a. a) Explain the operation of Buck and Boost inverter with suitable diagrams (6M)
b. b) What are the steps taken for designing inverter circuit (6M)

***** END *****