

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**B.Tech II Year I Semester Regular Examinations Nov/Dec 2019**
ELECTRONIC DEVICES
(ECE)

Time: 3 hours

Max. Marks: 60

PART-A(Answer all the Questions **5 x 2 = 10** Marks)

- 1 **a** Draw the ac equivalent circuit of a diode and mention any two applications of a PN junction diode. **2M**
- b** Define Ripple Factor and Efficiency of Half Wave Rectifier. **2M**
- c** In a common base connection, $I_C = 0.95$ mA and $I_B = 0.05$ mA. Find the value of α . **2M**
- d** What are the salient features of hybrid parameters? **2M**
- e** Compare BJT and FET. **2M**

PART-B(Answer all Five Units **5 x 10 = 50** Marks)**UNIT-I**

- 2 **a** Illustrate the formation of a p-n junction diode and explain the V- I characteristics. **5M**
- b** A silicon diode at Room temperature conducts 5 mA at 0.7 Volts. If the voltage increases to 0.8 Volts. Find forward, reverse saturation currents, and interpret the results. **5M**

OR

- 3 Draw the basic circuit diagram of a clamper and explain different types of clampers with the help of input and output waveforms. **10M**

UNIT-II

- 4 **a** Draw the circuit diagram of FWR with inductor filter and explain **5M**
- b** Design a bridge rectifier circuit, with the following specifications: **5M**
The transformer is connected to 220 Volts, 60 Hz mains and the turns ratio of the step down transformer is 11:1. Assume the diodes to be ideal, $R_L = 300$ k Ω . Calculate
(i) Voltage across the load (ii) Load current (iii) PIV

OR

- 5 **a** With a simple circuit, explain how Zener diode will act as a regulator. **5M**
- b** Discuss the principle of operation of a Varactor diode with suitable diagrams. **5M**

UNIT-III

- 6 Describe a set up to obtain the Input the Output characteristics of a transistor in CE configuration. Indicate and explain various regions of operation of the transistor. **10M**

OR

- 7 **a** List the various techniques of biasing a Transistor and explain any one technique. **5M**
- b** What is thermal runaway? Explain necessary conditions for a transistor to be in stable condition. **5M**

UNIT-IV

- 8 a Why hybrid model is used for the analysis of BJT amplifier at low frequencies? Draw hybrid model for CE transistor and derive the parameters. **6M**
b A voltage source of internal resistance $R_s = 900\Omega$ drives a CC amplifier using load resistance $R_L = 2000\Omega$. The CE h parameters are $h_{fe} = 60$, $h_{ie} = 1200\Omega$, $h_{oe} = 25\mu A/V$ and $h_{re} = 2 \times 10^{-4}$. Compute A_I , R_i , A_v and R_o using approximate analysis. **4M**

OR

- 9 a Determine the parameters A_I , R_i , A_v and R_o of Emitter Follower using simplified hybrid model analysis. **5M**
b Construct the circuit diagram of a single stage RC coupled Amplifier and discuss the steps used for designing it. **5M**

UNIT-V

- 10 a Explain the Drain & Transfer characteristics of a JFET. **5M**
b Draw the circuit diagram of common source amplifier and derive equation for gain of the amplifier. **5M**

OR

- 11 List and explain the steps involved in the manufacturing process of monolithic ICs. **10M**

END