

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)
B.Tech II Year I Semester Supplementary Examinations Nov/Dec 2019
BASIC ELECTRICAL & ELECTRONICS ENGINEERING
(CSE, CSIT & AGE)**

Time: 3 hours

Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART-A**UNIT-I**


- 1 a Define and Explain about ohms law. 5M
b Derive the expression for delta to star transformation for a resistive network. 5M

OR

- 2 a Find the RMS value of a sine wave. 5M
b Find the average value of a sine wave. 5M


UNIT-II

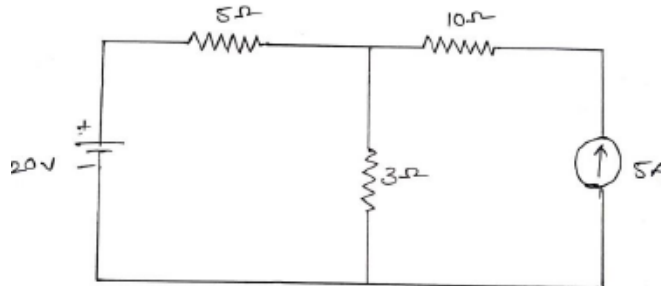- 3 Find the current passing through 3Ω Resistor for the circuit shown below in Fig by using Superposition Theorem? 10M



OR

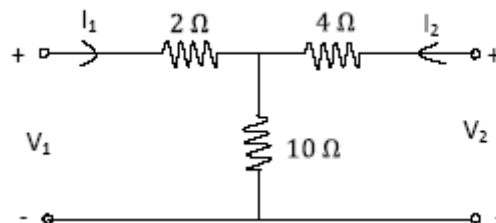- 4 a Find the transmission parameters for the network shown below. 5M



- b Define and explain about Impedance parameters. 5M

UNIT-III

- 5 a Derive Torque equation of dc motor. 5M
b Calculate the value of Torque established by the armature of a 4-pole motor having 774 conductors, 2 paths in parallel, 24mwb flux per pole when the total armature current is 50A. 5M

OR

- 6 a Explain principle of operation of transformer. 5M
b Explain different losses in a transformer. 5M

PART-B**UNIT-IV**

- 7 a With a neat sketch explain the operation of Half-wave rectifier. 5M
b Derive an expression for ripple factor of a Half- wave rectifier. 5M

OR

- 8 a Compare N-type and P-type semiconductor. 5M
b Define drift and diffusion currents. 5M

UNIT-V

- 9 a Explain the working of the CB configuration of a BJT. 5M
b Derive the relationship between α and β of BJT configurations. 5M

OR

- 10 a Describe the construction and explain the operation of depletion mode MOSFET. 5M
b Draw the static characteristics of MOSFET. 5M

UNIT-VI

- 11 a List out the classification of oscillators circuits. 5M
b State the Barkhausen conditions for sinusoidal oscillation. 5M

OR

- 12 a Explain the differential amplifier. 5M
b Explain the applications of OP-AMPS. 5M

***** END *****