

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations Dec 2019

PULSE AND DIGITAL CIRCUITS

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Explain the operation of RC Differentiator circuit and sketch the response for step input. **7M**
- b If a Pulse of 5V amplitude and pulse width of 0.5msec is applied to High Pass RC circuit consisting of $R=22K\Omega$ and $C=0.47 \mu F$, Calculate % Tilt of the output waveform. **5M**

OR

- 2 a Explain the response of RC low pass circuit for exponential input signal **6M**
- b A symmetrical square wave of amplitude $\pm 5v$ and frequency of 2 KHz is impressed on an RC low pass circuit. If $R= 5K\Omega$, $C=0.1\mu f$, Calculate and plot the steady state output with respect to time. **6M**

UNIT-II

- 3 a Draw the basic circuit diagram of positive peak clamper circuit and explain its operation. **6M**
- b Explain the effect of diode characteristics on clamping voltage. **6M**

OR

- 4 a Draw the diode comparator circuit and explain the operation when ramp input signal is applied. **6M**
- b Write short notes on **6M**
- I. Diode switching times
- II. Synchronized clamping.

UNIT-III

- 5 a Design a free running multivibrator to generate a square wave of amplitude 10 V and frequency of 1 KHz with 70% duty cycle. **7M**
- b Apply appropriate triggering technique to a collector coupled bistable multivibrator and explain briefly. **5M**

OR

- 6 a With the help of neat circuit diagram, Explain the working of Collector- Coupled one-shot multivibrator. **7M**
- b Design a Collector-Coupled one-shot multivibrator with the following specifications. Output pulse duration=500 m sec , $h_{FE(min)}= 25$, $I_c(sat) = 5 \text{ mA}$, $V_{CC}= 10 \text{ V}$, $V_{BB}= - 4 \text{ V}$, $V_{CE(sat)}= 0.4 \text{ V}$, $V_{BE(sat)} = 0.8 \text{ V}$. **5M**

UNIT-IV

- 7 a In a current sweep circuit, explain how linearity correction is made through adjustment of driving waveform. **7M**
- b Write the basic mechanism of transistor television sweep circuit. **5M**

OR

- 8 a Explain the basic principles of the miller and bootstrap time base generators. 6M
- b With the help of neat circuit diagram and waveforms, explain the working of a transistor constant current sweep circuit. 6M

UNIT-V

- 9 a What is sampling gate? Explain how it differs from Logic gates. 4M
- b What is pedestal? How it affects the output of a sampling gates. 5M
- c What are the drawbacks of two diode sampling gate? 3M

OR

- 10 a With the help of neat circuit diagrams and truth table explain the working of a DTL and RTL NAND gate. 6M
- b Compare the different logic families in terms of propagation delay, power dissipation, Noise margin, fan-in and fan-out. 6M

*** END ***