

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.TECH EEE II Year II Semester Supplementary Examinations May 2018

ANALOG ELECTRONIC CIRCUITS

(ELECTRICAL & ELECTRONICS ENGINEERING)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 X 12 = 60 Marks)

UNIT-I

- 1 a. Draw the block diagram of nth-stage cascaded Amplifier and derive voltage gain and current gain. 6M
b. Analyze the two stage RC coupled amplifier using FET with neat diagram. 6M

OR

- 2 a. Explain about
i) Half power Bandwidth ii) Decibels iii) Logarithm iv) Gain -band width product 12M

UNIT-II

- 3 a. Enumerate the effects of negative feedback on the various characteristics of the amplifier. 8M
b. What are the disadvantages of negative feedback amplifiers? 4M

OR

- 4 a. Draw the block diagram of an amplifier with feedback and explain its concept. 6M
Derive the stabilization gain of negative feedback amplifier 6M

UNIT-III

- 5 a. In Colpitts oscillator, $C_1 = 0.2 \mu\text{F}$ and $C_2 = 0.02 \mu\text{F}$. if the frequency of the oscillator is 10 KHz, find the value of the inductor. Also find the required gain for oscillation. 6M
b. Draw the circuit diagram of Colpitts oscillator and explain its working. 6M

OR

- 6 a. Draw the circuit diagram of Wien- bridge oscillator and explain its working. 6M
b. In a Wien – bridge oscillator, if the value of R is 100 K Ω , and frequency of oscillations is 10 kHz, Find the value of capacitor C. 6M

UNIT-IV

- 7 a. What are the types of Heat sinks and Explain the concept of power dissipation thermal stability. 5M
b. Determine the power dissipation capability of a transistor which has been mounted with a heat sink having thermal resistance $\Theta_{\text{HS-A}} = 8^{\circ}\text{C/W}$, $T_A = 40^{\circ}\text{C}$, $T_j = 160^{\circ}\text{C}$, $\Theta_{\text{j-A}} = 85^{\circ}\text{C/W}$. 7M

OR

- 8 a. Explain about Power dissipation thermal stability for a transistor. 6M
b. In a class B amplifier, $V_{\text{CE}}(\text{min}) = 2\text{V}$ and supply voltage $V_{\text{CC}} = 15\text{v}$. Find the collector circuit efficiency. 6M

UNIT-V

- 9 a. A 10Hz square wave is fed to an amplifier. Calculate and plot the output waveform under the following conditions: The lower 3 dB frequency is
i) 0.3 Hz ii) 3 Hz iii) 30 Hz 9M
b. Write a note on free running multivibrator. 3M

OR

- 10 a. Draw and explain a high pass RC circuit with neat sketch. List features and applications. 6M
b. Determine the upper 3-dB frequency for low pass RC circuit, if a pulse of 0.4 μsec is required to pass without distortion. Find the value of resistance if the capacitor is 0.001 μF . 6M

END