

**Reg. No:**

--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year I Semester Regular & Supplementary Examinations Nov/Dec 2018**

**DIGITAL LOGIC DESIGN**

(CSE,CSIT)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

**UNIT-I**

**1** Explain the Binary codes with examples? 12M

**OR**

- 2 a** Convert the following numbers 7M
- i)  $(41.6875)_{10}$  to Hexadecimal number
  - ii)  $(11001101.0101)_2$  to base-8 and base-4
  - iii)  $(4567)_{10}$  to base2
- b** Subtract  $(111001)_2$  from  $(101011)$  using 1's complement. 5M

**UNIT-II**

- 3 a** Implement the circuit by Using NAND gates  $F = ABC' + DE + AB'D'$  7M
- b** Implement the function  $F = (X+Y) \cdot (X'+Y'+Z')$  by Using NOR gates 5M

**OR**

**4** Simplify the Boolean expression using K-map. 12M  
 $F(A,B,C,D,E) = \sum m(0,1,4,5,16,17,21,25,29)$

**UNIT-III**

- 5 a** Implement the following Boolean function using 8:1 multiplexer. 7M  
 $F(A,B,C,D) = \sum m(0,1,2,5,7,8,9,14,15)$
- b** Explain about Decimal Adder. 5M

**OR**

- 6 a** Design a 4 bit adder-subtractor circuit and explain the operation in detail 7M
- b** Explain the functionality of a Multiplexer. 5M

**UNIT-IV**

- 7 a** Explain the Logic diagram of JK flip-flop. 7M
- b** Write difference between Combinational & Sequential circuits 5M

**OR**

- 8 a** Construct the PLA using the conversion from BCD code to Excess-3 code 7M
- b** Explain about Hamming Code with example. 5M

**UNIT-V**

**9** Encode the 11-bit code 10111011101 into 15 bit information code. 12M

**OR**

- 10 a** Differentiate among ROM, PROM, DROM, EPROM, EEPROM, RAM. 7M
- b** Explain about memory decoding. 5M

\*\*\* END \*\*\*