

Reg. No:

--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations June 2019

NETWORK ANALYSIS & SYNTHESIS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60


(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

- 1 a Derive the relation between phase and line quantities in a 3-phase balanced Delta connected system with the help of phasor diagram. 6M
- b An unbalanced 4 wire star connected load has a balanced voltage of 400 V. The loads are $Z_1=(4+j8) \Omega$, $Z_2=(5+j4) \Omega$, $Z_3=(15+j20) \Omega$. Calculate line currents, current in neutral wire, total power consumed by the load. 6M


OR

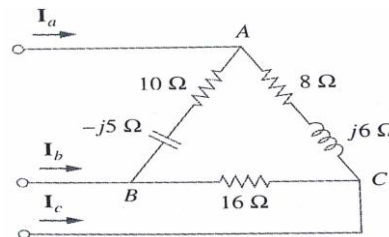- 2 a Derive the relation between phase and line quantities in a 3-phase balanced Star connected system with the help of phasor diagram. 6M
- b The circuit shown in Figure with an unbalanced Delta connected load is supplied by balanced line to line voltage 440 V in positive sequence. Find line currents when V_{ab} taking as reference. 6M



UNIT-II

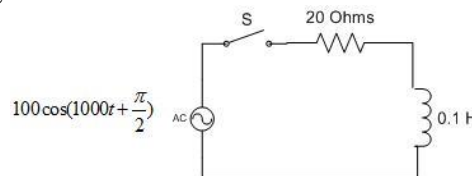- 3 a For the circuit shown in Figure find the current when the switch is closed at $t=0$. 6M




- b Derive the transient response of an RC circuit with DC excitation. 6M

OR

- 4 a A series RLC circuit with $R=20 \Omega$, $L=0.05 \text{ H}$ and $C=20 \mu\text{F}$ has a constant voltage 100V applied at $t=0$. Using Laplace transforms, find the current transient assuming zero initial conditions. 7M
- b Derive the transient response of an RL circuit with AC excitation. 5M


UNIT-III

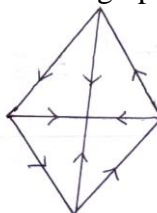- 5 a Define the following terms with suitable example 8M
(i) Tree (ii) Co-tree (iii) Oriented graph (iv) Fundamental loop
- b Determine the fundamental tie set matrix of the graph shown in Figure 4M




OR

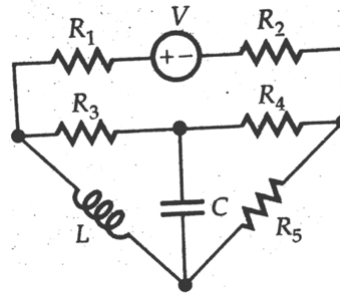- 6 a Develop the dual network of the circuit shown in Figure. 6M




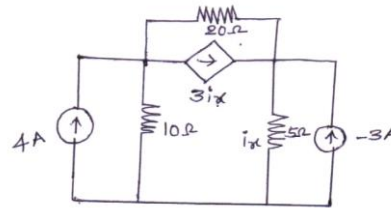- b Determine i_x for the following network using network topology of the network shown in Figure. 6M




UNIT-IV

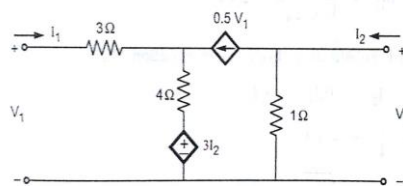- 7 a Express y-parameters in terms of transmission parameters for a two port network. 6M
 b Calculate 'h' parameters of the network shown in Figure. 6M



OR

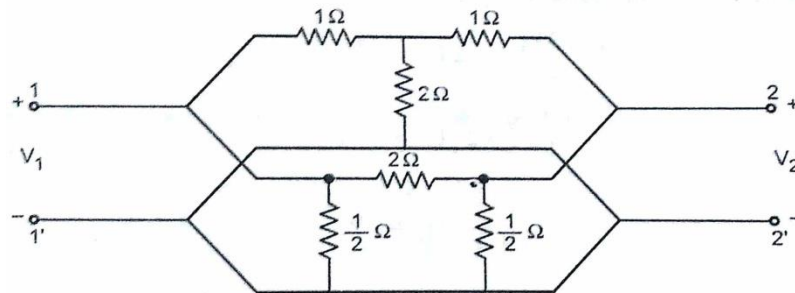- 8 a Determine Y- parameters of the network shown in Figure. 6M



- b Express Z-parameters in terms of h-parameters for a two port network. 6M

UNIT-V

- 9 a Derive the design equations of m-derived high pass filter 5M
 b Design K-type band pass filter having a design impedance of 500 Ω and cut-off frequencies $f_1=1\text{Khz}$ and $f_2=10\text{Khz}$ 7M

OR

- 10 a Design a π -type attenuator to give 20 dB attenuation and to have a characteristic impedance of 100 Ω. 6M
 b Design a T- pad attenuator to give an attenuation of 60 dB and to work in line of 500 Ω impedance. 6M

*** END ***