

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Regular & Supplementary Examinations May 2019**

**ANALOG ELECTRONIC CIRCUITS**

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

**UNIT-I**

- 1 Draw the block diagram of two stage RC coupled using FET amplifier and its frequency response. 12M

**OR**

- 2 a Derive the equation for the overall voltage gain of a multistage amplifier in terms of the individual voltage gains. 6M  
b Compare various coupling schemes used in amplifiers. 6M

**UNIT-II**

- 3 a What are the characteristics of negative feedback amplifier? Explain. 6M  
b An amplifier has voltage gain with feedback of 100. If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%, determine the value of open loop gain A and feedback ratio  $\beta$ . 6M

**OR**

- 4 Derive the expression for input impedance and output impedance for the current series and current shunt feedback amplifiers. 12M

**UNIT-III**

- 5 a Draw the circuit diagram of RC phase shift Oscillator and Explain its working. 7M  
b State and explain Barkhausen criterion of Oscillations. 5M

**OR**

- 6 a Draw the circuit of Hartley oscillator and explain its working. Derive the expressions for frequency of oscillation. 7M  
b In a Hartley oscillator,  $L_2 = 0.4$  mH and  $C = 0.004$   $\mu$ F. If the frequency of the oscillator is 120kHz, find the value of  $L_1$ . Neglect the mutual inductance. 5M

**UNIT-IV**

- 7 a Explain the classification of amplifiers based on the biasing condition. 5M  
b Show the conversion efficiency of transformer coupled class A amplifier is 50%. 7M

**OR**

- 8 a Draw the circuit diagram of complementary symmetry class B amplifier and explain its working principle. 6M  
b What are the Advantages & disadvantages of complementary symmetry class B amplifier. 6M

**UNIT-V**

- 9 a Derive the Response of a low pass RC circuit for Step input. 7M  
b Determine the upper 3-dB frequency for low pass RC circuit, if a pulse of 0.4  $\mu$ sec is required to pass without distortion. Find the value of resistance if the capacitor is 0.001 $\mu$ F. 5M

**OR**

- 10 a A 10Hz square wave is fed to an amplifier. Calculate and plot the output waveform under the following conditions: The lower 3 dB frequency is  
i) 0.3 Hz    ii) 3 Hz    iii) 30 Hz 7M  
b Write a note on free running multivibrator. 5M

\*\*\* END \*\*\*