

Reg. No:

| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|
| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Regular & Supplementary Examinations Nov/Dec 2019

SWITCHING THEORY AND LOGIC DESIGN

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Convert the given decimal number 234 to binary, octal, hexadecimal and BCD equivalent. **6M**
 b Simplify the following Boolean expressions using the Boolean theorems **6M**
 i) $(A+B+C)(B'+C)(A'+C)$
 ii) $(A+B)(A+B')(A'+B)$

OR

- 2 a Solve for x **6M**
 i) $(257)_8 = (x)_2$
 ii) $(BC2)_{16} = (x)_8$
 iii) $(33)_{10} = (201)_x$
 b Express the decimal digits 0-9 in BCD, 2421 and Excess-3 codes. **6M**

UNIT-II

- 3 a Simplify the given Boolean function using map method. **8M**
 $F(A,B,C,D,E) = \Sigma m(0,2,4,6,9,13,21,23,25,29,31)$.
 b Implement the AND and OR gates by using NOR gates only. **4M**

OR

- 4 a Simplify the Boolean function by using tabulation method. **8M**
 $F(A,B,C,D) = \Sigma m(1,3,5,8,9,11,15)$.
 b Simplify the given Boolean function using map method. **4M**
 $F(x, y, z) = \Sigma m(0,1,2,3,7)$.

UNIT-III

- 5 a Design and Implement Half subtractor and Full subtractor with truth tables. **6M**
 b Draw and explain the operation of three bit magnitude comparator. **6M**

OR

- 6 a What is encoder? Design octal to binary encoder. **6M**
 b Design a 16 line to 1 line multiplexer using 4 line to 1 line multiplexer. **6M**

UNIT-IV

- 7 a Explain and design the 4-Bit Asynchronous Ripple down counter. **8M**
 b Write the differences between combinational and sequential circuits. **4M**

OR

- 8 a What is race around problem in JK Flip-Flop? Explain how it is eliminated in master slave JK Flop-Flop. **6M**
 b Show that how ring counter acts as a Johnson counter. **6M**

UNIT-V

- 9 a** Implement the following three Boolean functions with a PLA: **6M**
 $F1(A,B,C)=\sum(0,1,2,4);$
 $F2(A,B,C)=\sum(0,5,6,7);$
 $F3=\sum(0,3,5,7).$
- b** Design a combinational circuit using a ROM. The circuit accepts a three-bit number **6M**
and outputs a binary number equal to the square of the input number.
- OR**
- 10 a** Implement the following Boolean function using PAL with AND-OR structure **8M**
 $F1(A,B,C,D)=\sum m(2,12,13);$
 $F2(A,B,C,D)=\sum m(7,8,9,10,11,12,13,14,15)$
 $F3(A,B,C,D)=\sum m(0,2,3,4,5,6,7,8,10,11,15);$
 $F4(A,B,C,D)=\sum m(1,2,8,12,13).$
- b** Explain about Mealy and Moore models of sequential circuits. **4M**

*** END ***