

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech III Year I Semester Regular & Supplementary Examinations Nov/Dec 2019
POWER ELECTRONICS
(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

1 Draw and explain V-I characteristics of SCR and its working. **12M**

OR

- 2 a** A bipolar transistor has current gain $\beta = 40$. The load resistance $R_c = 10 \text{ ohm}$, dc supply voltage $V_{CC} = 130\text{v}$ and input voltage to base circuit $V_B = 10\text{v}$. For $V_{CES} = 1\text{v}$ and $V_{BES} = 1.5\text{v}$ calculate **12M**
- a) The value of R_B for operation in the saturated state
 - b) The value of R_B for an over drive factor 5.
 - c) Forced current gain and
 - d) Power loss in the transistor.

UNIT-II

3 a Give the difference between midpoint and bridge type converters **6M**

b Give the difference between discontinuous mode and continuous mode of operation. **6M**

OR

- 4 a** A single phase half wave converter is operated from a 230V, 50Hz supply. If the load is Resistive of value 10 ohms and delay angle is 60° . Determine **12M**
- i) the rectification efficiency
 - ii) form factor
 - iii) ripple factor
 - iv) Transformer utilization factor
 - v) Peak inverse voltage of thyristor.

UNIT-III

5 Explain the operation of three phase dual converter with circulating current type. **12M**

OR

6 At firing angle of 120° , explain the operation of three phase fully controlled converter with RLE load with necessary waveform. **12M**

UNIT-IV

7 Explain about the 1 – ϕ AC voltage controller with RL loads with neat diagram **12M**

OR

8 Draw and explain bridge type cyclo-converter for discontinuous conduction mode. **12M**

UNIT-V

9 a Describe the principle of chopper operation. **6M**

b List out various control strategies for chopper. **6M**

OR

10 a What is series inverter? Explain it with neat circuit diagram. **8M**

b What are the applications of inverters? **4M**

*** END ***