

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations July-2022

ELECTRONIC CIRCUIT ANALYSIS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a With neat diagram, derive the CE amplifier parameters using approximate analysis. L2 6M
b Draw the h-parameter equivalent model for a BJT Amplifier in CE configuration. L2 6M

OR

- 2 a Compare the CE, CB and CC transistor amplifier parameters. L2 6M
b Draw the circuit diagram of JFET Common Source amplifier with voltage divider bias for bypassed R_s and determine the expression for input impedance, output impedance and voltage gain. L2 6M

UNIT-II

- 3 a Discuss the dependency of hybrid- π parameters upon collector current, V_{CE} and Temperature. L2 6M
b A BJT has the following parameters measured at $I_c=1mA$, $h_{ie}=3k\Omega$, $h_{fe}=100$, $C_c=2pF$ and $C_e=18pF$. Find g_m , $r_{b'e}$, and $r_{bb'}$ for $R_L=1 K\Omega$. L4 6M

OR

- 4 a Derive the expression for Hybrid- π capacitance of CE transistor at high frequency. L3 6M
b Describe the relationship between low frequency h-parameters and high frequency Parameters. L1 6M

UNIT-III

- 5 a What is Darlington Connection? Mention the advantages of Darlington Pair Amplifier. L1 4M
b With diagram, derive the expression for current gain and input resistance of Darlington amplifier. L2 8M

OR

- 6 a Explain the effect of cascading of amplifiers on bandwidth. L1 6M
b An amplifier consists of 3 identical stages in cascade, the bandwidth of overall amplifier extends from 20 Hz to 20 kHz. Calculate the bandwidth of individual stage. L4 6M

UNIT-IV

- 7 a Discuss various Feedback topologies with neat diagrams. L1 8M
b Derive the expressions of input and output resistances for Voltage Series Feedback Amplifier. L3 4M

OR

- 8 a Derive the expression for frequency of oscillations for RC phase shift Oscillator. L4 8M
b State Barkhausen Criterion for oscillations. Explain the principle of operation of oscillator. L1 4M

UNIT-V

- 9 a Describe Complementary Symmetry Class B Power Amplifier with diagram and write about crossover distortion in class B power amplifiers. **L1 6M**
- b A class B push pull amplifier supplies power to a resistive load of 12Ω . The output transformer has a turns ratio of 3:1 and efficiency of 78.5%. Obtain (i) Maximum power output, (ii) maximum power dissipation in each transistor and (iii) Maximum base and collector current. For each transistor, assume $h_{fe} = 25$ and $V_{CC} = 20V$. **L4 6M**

OR

- 10 a Write notes on Class AB operation. **L1 6M**
- b Discuss the need of Heat sink for power transistors. Mention about thermal stability of power transistors. **L2 6M**

*** END ***