

Reg. No: 

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech II Year II Semester Supplementary Examinations July-2022**

**POWER ELECTRONICS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- |   |   |  |    |    |
|---|---|--|----|----|
| 1 | a | Define Latching current.   | L2 | 2M |
|   | b | What is Transformer utilization factor?                            | L1 | 2M |
|   | c | What are the applications of dc chopper?                           | L1 | 2M |
|   | d | What is meant by PWM control?                                      | L2 | 2M |
|   | e | What are the applications of Three phase voltage source inverters? | L2 | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |           |   |    |     |
|-----------|---|----|-----|
| 2         | Explain briefly voltage commutation and Draw the output wave forms.   | L2 | 10M |
| <b>OR</b> |   |    |     |
| 3         | Briefly explain Metal oxide semiconductor field effect transistor (MOSFET) and its switching characteristics. | L3 | 10M |

**UNIT-II**

- |           |   |    |     |
|-----------|---|----|-----|
| 4         | Explain the operation of single phase Full wave converter with R-Load with necessary Wave forms. Also, derive the output voltage, output current and RMS output voltages. | L3 | 10M |
| <b>OR</b> |   |    |     |
| 5         | Explain the operation of single phase half wave converter with RL-Load with necessary waveforms. Also derive the output voltage, output current and RMS output voltages.  | L1 | 10M |

**UNIT-III**

- |           |  |    |     |
|-----------|--|----|-----|
| 6         | What is a dc chopper? Describe various types of chopper configurations with neat sketch.       | L2 | 10M |
| <b>OR</b> |  |    |     |
| 7         | Explain the boost converter operation with help of diagram and also draw the output waveforms. | L2 | 10M |

**UNIT-IV**

- |           |   |    |     |
|-----------|---|----|-----|
| 8         | Analyze the single-phase half bridge Voltage Source Inverter and perform steady state analysis? | L4 | 10M |
| <b>OR</b> |   |    |     |
| 9         | Explain briefly single Phase Pulse width modulation with neat diagrams.                         | L2 | 10M |

**UNIT-V**

- |           |  |    |     |
|-----------|--|----|-----|
| 10        | Explain the three-phase Voltage Source Inverter with $120^\circ$ conduction mode. Also derive the output voltage and output current?   | L3 | 10M |
| <b>OR</b> |  |    |     |
| 11        | A 1- $\phi$ bridge inverter delivers power to a series connected RLC load with $R=2\Omega$ and $\omega L=10\Omega$ . The periodic time $T=0.1$ msec. What value of C should the load have in order to obtain load commutation for the SCRs. The thyristor turn off time is $10\mu\text{sec}$ . Take circuit turn off time as $1.5 t_q$ . Assume that load current contains only fundamental component. | L3 | 10M |

\*\*\*END\*\*\*