

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations July-2021

DIGITAL LOGIC DESIGN

(Common to CSE & CSIT)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | |
|---|---|----|
| 1 | a Which gates are called as the universal gates? What are its advantages? | 2M |
| | b What are called don't care conditions? | 2M |
| | c Write any two differences between encoder and decoder. | 2M |
| | d What is state diagram? | 2M |
| | e List the major differences between PLA and PAL. | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | |
|---|--|----|
| 2 | a Determine the value of base x if $(211)_x = (152)_8$ | 5M |
| | b Explain the Excess-3 code? Write about Error correction & Detection. | 5M |

OR

- | | | |
|---|---|----|
| 3 | a State and Explain the DeMorgan's Theorem and Consensus Theorem. | 5M |
| | b Explain the Binary codes with examples. | 5M |

UNIT-II

- | | | |
|---|--|-----|
| 4 | Simplify the Boolean expression using K-MAP
$F(A,B,C,D) = \sum m(1,2,3,8,9,10,11,14) + d(7,15)$ | 10M |
|---|--|-----|

OR

- | | | |
|---|---|-----|
| 5 | Simplify the Boolean expression using K-map.
$F(A,B,C,D,E) = \sum m(0,2,4,6,9,11,13,15,17,21,25,27,29,31)$ | 10M |
|---|---|-----|

UNIT-III

- | | | |
|---|---|----|
| 6 | a Implement the following Boolean function using 8:1 multiplexer.
$F(A,B,C,D) = \sum m(0,1,2,5,7,8,9,14,15)$ | 5M |
| | b Explain about Binary Multiplier. | 5M |

OR

- | | | |
|---|---|----|
| 7 | a Design the combinational circuit of 4 Bit Parallel Adder. | 5M |
| | b Explain full binary subtractor in detail. | 5M |

UNIT-IV

- | | | |
|---|---|----|
| 8 | a Draw and explain the operation of SR LATCH. | 5M |
| | b Explain about Ring counter. | 5M |

OR

- | | | |
|---|---|-----|
| 9 | Design 4-bit binary synchronous counter with D-flip flop. | 10M |
|---|---|-----|

UNIT-V

- | | | |
|----|---|-----|
| 10 | Construct the PROM using the conversion from BCD code to Excess-3 code. | 10M |
|----|---|-----|

OR

- | | | |
|----|-----------------------------|----|
| 11 | a Explain about TTL family. | 5M |
| | b Explain about CMOS Logic. | 5M |

END