

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations July-2021

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to CE & AGE)

Time: 3 hours

Max. Marks:60

(Answer all Six Units 6 X 10 = 60Marks)


PART-A

UNIT-I

- 1 a Explain about basic circuit components in detail. 5M
 b Explain about KVL. 5M

OR

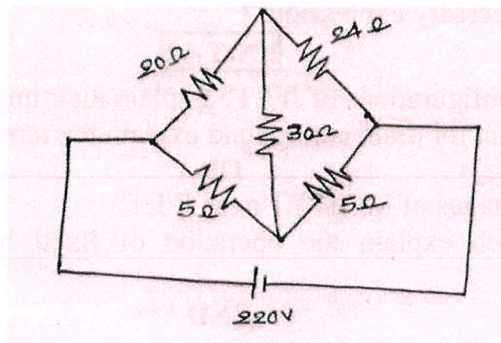- 2 Find the current delivered by the source for the circuit shown in figure. 5M




UNIT-II

- 3 a Define and explain about Impedance parameters 5M
 b Define and explain about Y- parameters 5M

OR

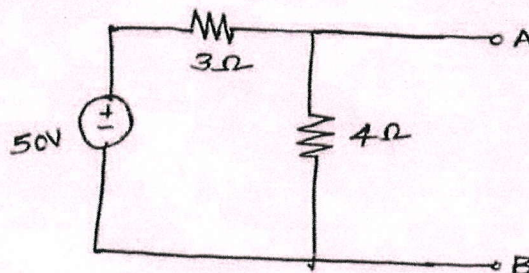- 4 a State Norton's theorem 2M
 b Find Norton's equivalent circuit across AB for the circuit shown in below 8M



UNIT-III

- 5 a Explain about principle of operation of DC Motors in detail. 5M
 b Calculate the value of Torque established by the armature of a 4-pole motor having 774 conductors, 2 paths in parallel, 24 mwb flux per pole when the total armature current is 50A. 5M

OR

- 6 a Derive EMF equation of a transformer 5M
 b 100KVA, 11000V/400V, 50Hz transformer has 40 secondary turns. Calculate the number of primary turns and primary and secondary currents. 5M

PART-B**UNIT-IV**

7 Explain how current flows in a PN diode? With a neat sketch explain the VI characteristics of the diode? **10M**

OR

8 a With a neat sketch explain the operation of Full-wave rectifier? **5M**

b Derive an expression for ripple factor of a Half-wave rectifier with and without load? **5M**

UNIT-V

9 a With a neat sketch explain the construction and working principle of NPN transistor? **4M**

b Draw the Output Characteristics of NPN transistor? Explain the operation of NPN transistors in three regions specified in the output characteristics? **6M**

OR

10 Draw input and output characteristics CE configuration? Explain the Operation of CE transistor with necessary expressions? **10M**

UNIT-VI

11 a Sketch different configurations of JFET? Explain their importance in electronics? **5M**

b Write the expression for drain current and explain the terms? **5M**

OR

12 a Discuss the Advantages of MOSFET over JFET? **5M**

b With a neat sketch explain the operation of fixed bias configuration using MOSFET? **5M**

***** END *****