

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations July-2021

DIGITAL LOGIC DESIGN

(Common to CSE & CSIT)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Convert the following numbers 3M
- i) $(AB)_{16} = ()_2$
- ii) $(1234)_8 = ()_{16}$
- iii) $(101110.01)_2 = ()_8$
- b Convert the following to binary and then to gray code $(AB33)_{16}$ 4M
- c Perform the following Using BCD arithmetic $(7129)_{10} + (7711)_{10}$ 5M

OR

- 2 a Simplify the Boolean expressions to minimum number of literals 6M
- (i) $X' + XY + XZ' + XYZ'$
- (ii) $(X+Y)(X+Y')$
- b Express the Boolean function $F=A+B'C$ as a sum of minterms. 6M

UNIT-II

- 3 a Simplify the Boolean expression using K-map method 6M
- $F(A,B,C,D) = \sum m(1,2,3,8,9,10,11,14) + d(7,15)$
- b Design the circuit by Using NOR gates $F = (X+Y) \cdot (X'+Y'+Z')$ 6M

OR

- 4 a Simplify the following Boolean expression using K-MAP and implement using NAND gates. $F(W,X,Y,Z) = XYZ+WXY+WYZ+WXZ$ 7M
- b Reduce the expression $F(A,B,C,D) = \pi M(0,2,7,8,9,10,11,15) \cdot d(3,4)$ using K-Map. 5M

UNIT-III

- 5 a Draw and explain the working of a Carry- Look- a-head adder. 6M
- b Implement the following Boolean function using 8:1 multiplexer 6M
- $F(A, B, C, D) = A'BD' + ACD + A'C'D + B'CD$

OR

- 6 a Explain about Decimal Adder. 7M
b Design and draw a full adder circuit. 5M

UNIT-IV

- 7 a Draw and explain the operation of D Flip-Flop? 6M
b Explain about Shift Registers? 6M

OR

- 8 a What is race-around condition? How does it set eliminate is a Master –slave J-K flip-flop? 6M
b Explain the design of a 4 bit binary counter with parallel load in detail. 6M

UNIT-V

- 9 a Construct the PROM using the conversion from BCD code to Excess-3 code. 6M
b What is ROM. List the different types of ROMs. 6M

OR

- 10 Design a Combinational circuit using PAL by considering the following Boolean Functions given in sum of minterms: 12M

$$W(A,B,C,D)=\Sigma m (2,12,13)$$

$$X(A,B,C,D)=\Sigma m (7,8,9,10,11,12,13,14,15)$$

$$Y(A,B,C,D)=\Sigma m (0,2,3,4,5,6,7,8,10,11,15)$$

$$Z(A,B,C,D)=\Sigma m (1,2,8,12,13)$$

*** END ***