

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech I Year II Semester Supplementary Examinations July-2021

BASIC ELECTRICAL ENGINEERING
(Electronics and Communication Engineering)

Time: 3 hours


Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Determine the mesh currents for the circuit shown below.

6M

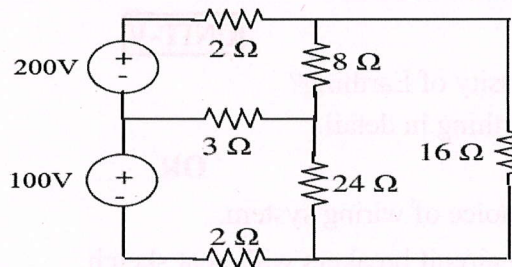

- b State & explain Super position theorem.

6M


OR

- 2 a Determine the Equivalent Resistance when the resistors are connected in Series & Parallel.

6M

- b Find the Thevenin's equivalent for the circuit shown below

6M

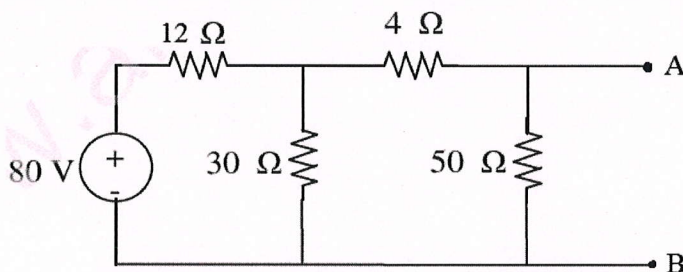

UNIT-II

- 3 a Derive an expression for RMS and AVERAGE values of sinewave form.

8M

- b An alternating current is expressed as $I = 14.14 \sin 314t$. Determine.

4M

Maximum current (ii) RMS current (iii) Frequency
(iv) Instantaneous current when $t = 0.04\text{msec}$.

OR

- 4 a Explain Resonance for series RLC circuit and derive the equation for resonant frequency.

8M

- b A series RLC circuit of $R=40\ \Omega$, $L= 50.07\text{mH}$ and a capacitor is connected across a 400V, 50Hz, A.C supply. This RLC combination draws a current of 10A. Calculate Power factor of the circuit and Capacitor value.

4M

UNIT-III

- 5 Explain the Constructional details of D.C machine with neat sketch. 12M
- OR**
- 6 a What is the necessity of speed control? 5M
b How to control the speed of D.C. Shunt motor. Explain it with any one example. 7M

UNIT-IV

- 7 a Derive an EMF equation of a single-phase transformer. 6M
b A single-phase transformer has 400 turns on primary winding 1000 turns on secondary winding. If it is operating at 50Hz supply with a maximum flux of 0.045Wb. Find (i) Primary & Secondary induced EMF (ii) EMF induced per turn. 6M
- OR**
- 8 Explain the Procedure for calculating the regulation of 3-Phase Alternator using Synchronous Impedance Method. 12M

UNIT-V

- 9 a What is the necessity of Earthing? 6M
b Explain Plate Earthing in detail. 6M
- OR**
- 10 a Explain about choice of wiring system. 6M
b Explain any two circuit breakers with neat sketch. 6M

*** END ***