

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

B.Tech I Year II Semester Supplementary Examinations July-2021

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to CSE, CSIT & AGE)

Time: 3 hours


Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART-A


UNIT-I

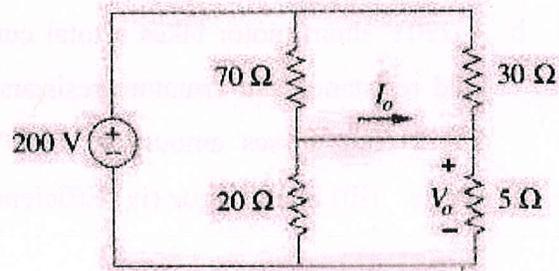- 1 a Explain in detail about passive elements. 5M
- b Find i_1, i_2, i_3 for the given circuit by using Kirchoff's laws? 5M




OR

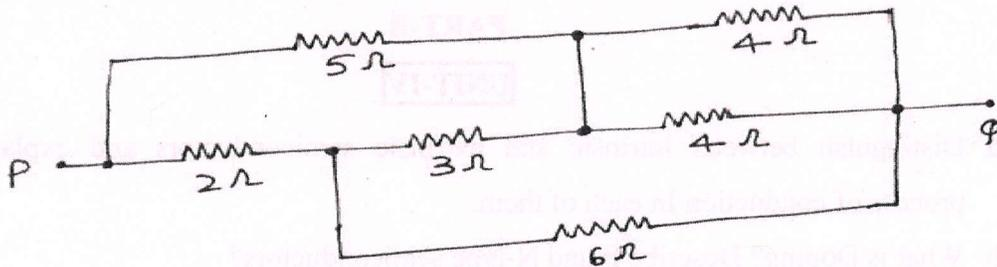- 2 a Define RMS value, average value, form factor and peak factor 5M
- b Determine the equivalent resistance in between the terminals P & Q: 5M



UNIT-II

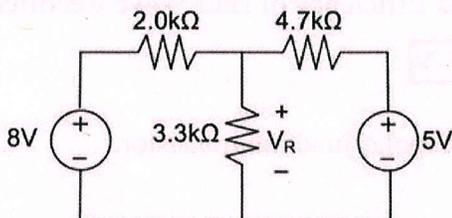
- 3 a State and explain Norton's theorem: 10M
- b



Determine the current flowing through 3.3kohm by using superposition theorem:

OR

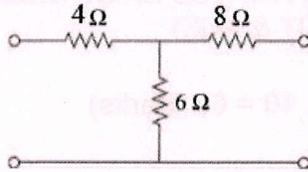- 4 a Explain about short circuit parameters: 5M
b 5M



Find the h- parameters for the following circuit.

UNIT-III

- 5 a Discuss about the principle of operation of DC motors 5M
b A 220V shunt motor takes a total current of 80A and runs at 800 r.p.m. Shunt field resistance and armature resistance are 50Ω and 0.1Ω , respectively. If iron and friction losses amount to 1600W. Find (i) Copper losses (ii) Armature torque (iii) Shaft torque (iv) Efficiency. 5M

OR

- 6 a Derive the condition for maximum efficiency of the transformer. 5M
b A 20 kVA, 2000/200 V, 50 Hz transformer has 66 secondary turns. Calculate the number of primary turns and primary and secondary currents. Neglect losses. 5M

PART-B

UNIT-IV

- 7 a Distinguish between intrinsic and extrinsic semiconductors and explain the process of conduction In each of them. 5M
b What is Doping? Describe P-and N-type semiconductors? 5M

OR

- 8 a Discuss Zener Diode breakdown mechanism. Draw the Zener diode in its reverse bias and explain its Volt-Ampere characteristics. 5M
b Derive the expression for Ripple factor and Efficiency of Half Wave Rectifier. 5M

UNIT-V

- 9 a Describe in detail the working of an NPN bipolar junction transistor. Why is it called Bipolar? 5M
b Draw the circuit diagram for a common base circuit arrangement and plot its 5M

input and Output characteristics. Show the different regions of the output characteristics and explain their occurrence.

OR

- 10** a Describe the Voltage Divider Bias Network of BJT with diagram and equations. **5M**
b Write the application of a transistor and explain the transistor acts a switch. **5M**

UNIT-VI

- 11** a Explain the construction and principle of operation of N-channel JFET: **5M**
b Define the JFET Volt-Ampere Characteristics and determine FET parameters: **5M**

OR

- 12** a Compare BJT and JFET. **5M**
b Draw the construction of EMOSFET and explain its operation: **5M**

***** END *****

