

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations August-2021

DIGITAL SYSTEM DESIGN

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- 1 a Why XS-3 code is called a self-complementing code? 2M
 b List the applications of MUX and DEMUX. 2M
 c Draw the MOD-2 Counter 2M
 d Realize $F(x,y,z) = \sum(1,2,5,7)$ using PLA. 2M
 e Write a VHDL Program for 2x4 Decoder in Dataflow Model 2M

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- 2 a Convert the following. 5M
 i) $(BC)_{16} = ()_{10}$
 ii) $(2314)_8 = ()_{10}$
 iii) $(1000011)_2 = ()_{10}$
 iv) $(647)_{10} = ()_{16}$
 v) $(292)_{10} = (1204)_b$
 b Express the following numbers in decimal. 5M
 (I) $(10110.0101)_2$
 (II) $(16.5)_{16}$
 (III) $(26.24)_8$
 (IV) $(BC54)_{16}$
 (V) $(323)_8$

OR

- 3 a Explain about the Binary Codes. 5M
 b Simplify the following Boolean functions to minimum number of literals. 5M
 i) $F = xy + x'z + yz$.
 ii) $F = x'y'z + x'yz + xy'$
 iii) $F = (x+y)'(x'+y')$
 iv) $F = xy + xy' + x'y$
 v) $F = (BC' + A'D)(AB' + CD')$

UNIT-II

- 4 a Simplify the following Boolean function for minimal SOP & POS form using K-map 5M
 $F(A, B, C, D) = \sum(0,1,2,5,8,9,10)$
 b Explain about carry look ahead adder with suitable diagram 5M

OR

- 5 a Obtain Product of sums form for $F = x'z' + y'z' + yz' + xy$ 5M
 b With a neat design procedure, explain the implementation of a 4-bit Magnitude Comparator. 5M

UNIT-III

- 6 a Explain the difference between Ring and Johnson counters with neat sketch 5M
 b Explain the operation of an SR Flip Flop using excitation table. Give its Truth Table and Characteristic Equation 5M

OR

- 7 a Design and implement a BCD Ripple counter using JK Flip Flops. 6M
b Give the characteristic table, Truth table, characteristic equation and excitation table for T and D Flip Flops. 4M

UNIT-IV

- 8 a What is meant by Tristate logic? Draw the circuit of Tristate TTL logic and explain the functions. 6M
b Derive the PLA programming table for the combinational circuit that squares a 3-bit number. 4M

OR

- 9 a Give the classification of integrated circuits and compare the various logic families 5M
b Compare three combinational circuits: PLA, PAL and ROM. 5M

UNIT-V

- 10 a Explain the importance of Schematic in VHDL. 5M
b Write a VHDL program for a 4X1 MUX. 5M

OR

- 11 a Explain about Simulation and Synthesis processes in VHDL 5M
b Write a VHDL program for 3 to 8 Decoder 5M

END