

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations August-2021

**ELECTRICAL CIRCUITS-II**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- 1 a Write the voltage and current relationship in Delta connected system. 2M
- b What is the transient response of RL series circuit with dc excitation? 2M
- c Define duality. 2M
- d Write the generalized equations for Y-Parameters. 2M
- e Define Transfer function. 2M

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- 2 a Explain active power measurement in balanced three phase load system. 5M
- b Derive the relationship between Phase and Line voltages, currents in delta connected load. 5M

OR

- 3 A 400V, 3- $\phi$  supply feeds an unbalanced 3 wire star connected 3 wire, star connected load. The branch impedances of the load are  $Z_R=(4+j8)\Omega$ ,  $Z_Y=(3+j4)\Omega$ ,  $Z_B=(5+j20)\Omega$ . Find the line currents and voltages across phase impedance. Assume RYB phase sequence. 10M

**UNIT-II**


- 4 a Derive the transient response of an RL circuit with dc excitation. 5M
- b Derive the transient response of an RC circuit with dc excitation. 5M

OR


- 5 A series RC circuit consists of resistor of 10 and capacitor of 0.1F has a constant voltage of 20v is applied to the circuit at  $t=0$ . obtain the current equation. Determine the voltage across the resistor and the capacitor. 10M

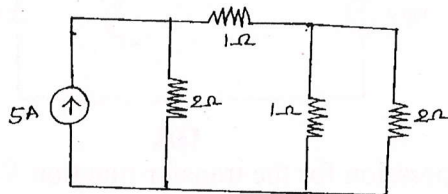**UNIT-III**

- 6 a Find the cutset matrix for the following? 5M



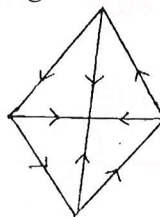
- b Find the cutset matrix for the following? 5M



OR

7 Determine mesh currents for the following network using network topology.


10M

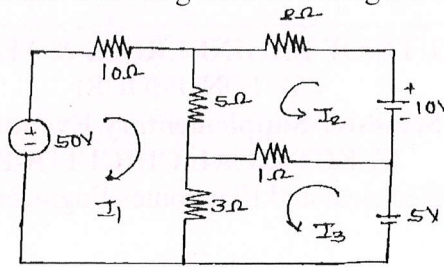

UNIT-IV

8 Find the Z - parameters for the resistance network shown in figure.


10M

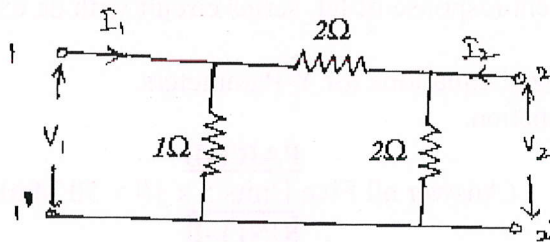

OR

9 Obtain the T parameters of the following two port network.

10M

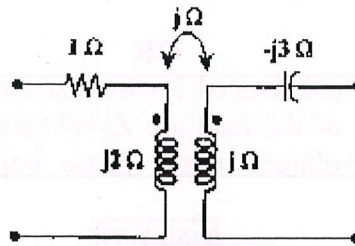


UNIT-V

10 The energy stored in the circuit shown is zero at the time when the switch is closed.

10M

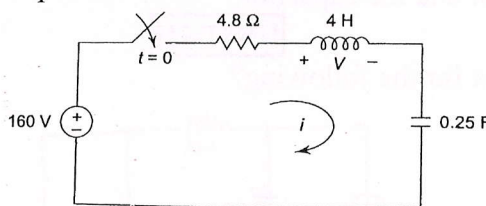
- (A) find the s- domain expression for  $I$
- (B) find the time domain expression for  $i$  when  $t > 0$ .
- (C) find the s- domain expression for  $V$ .
- (D) find the time domain expression for  $v$  when  $t > 0$ .



OR

11 Derive the numerical expression for the transfer function  $V_o / I_g$  for the circuit shown.

10M

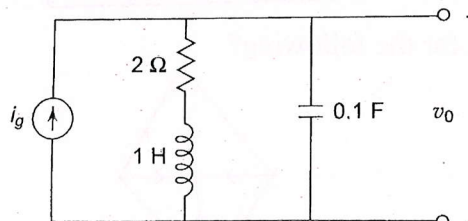

\*\*\*END\*\*\*