

Reg. No: 

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)

B. Tech II Year I Semester Supplementary Examinations August-2021

NETWORK THEORY

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)


- 1 a Write statement of Reciprocity theorem. 2M
- b Define Quality-factor and Selectivity. 2M
- c Define steady state and transient state 2M
- d Draw the equivalent circuit of Z-parameters. 2M
- e Define Fourier series. 2M

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

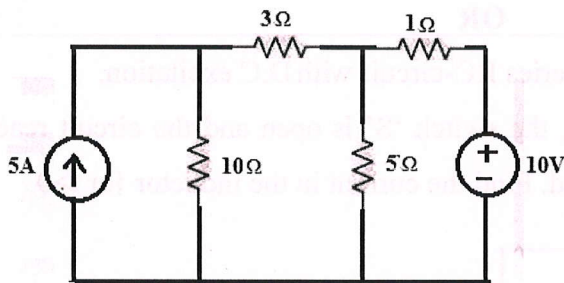
**UNIT-I**

- 2 a Explain about Mesh analysis and write the steps for writing mesh analysis. 5M
- b Determine the current in  $10\Omega$  resistor for the following network by using nodal analysis 5M



OR

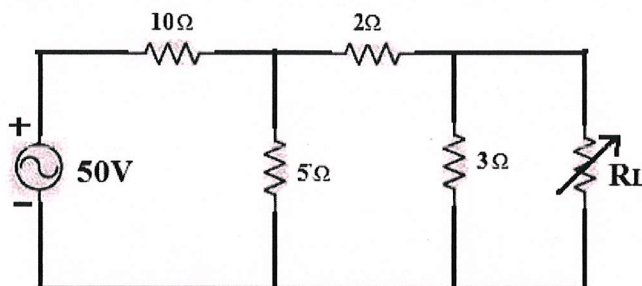- 3 a State and prove Maximum power transfer theorem. 5M
- b Determine the maximum power delivered to the load in the circuit shown in below figure 5M



## UNIT-II


- 4 a Explain about Quality factor and Bandwidth of Series resonance. 5M  
 b Design constant-K band pass filter having a design impedance of  $500\Omega$  and cut-off frequencies  $f_1 = 1\text{kHz}$  and  $f_2 = 10\text{kHz}$ . 5M

OR

- 5 a Design a High-pass filter having a cut-off frequency of  $1\text{kHz}$  with a load resistance of  $600\Omega$  5M  
 b Design Low Pass Filter in both T &  $\Pi$  section having a cut off frequency of  $2\text{kHz}$  to operate with a terminated load resistance of  $500\Omega$  5M

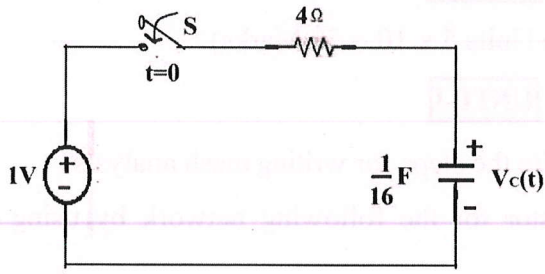
## UNIT-III

- 6 a Derive the Transient Response of series RL-circuit with D.C excitation. 5M  
 b Using classical method of solution of differential equations, find the value of  $V_c(t)$  for  $t > 0$  in the circuit shown in figure. Assume  $V_c(0^-) = 9\text{V}$ . 5M




OR

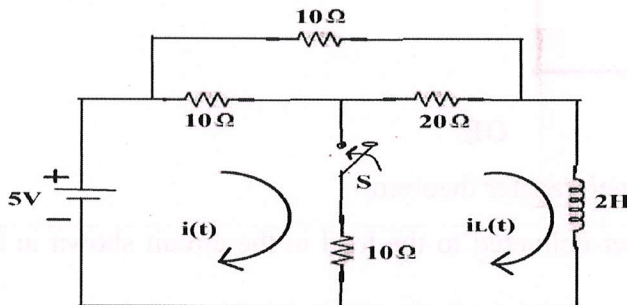- 7 a Derive the Transient Response of series RC-circuit with D.C excitation. 6M  
 b The circuit shown in below figure, the switch 'S' is open and the circuit reaches a steady state. At  $t=0$ , the 'S' is closed. Find the current in the inductor for  $t > 0$ . 4M



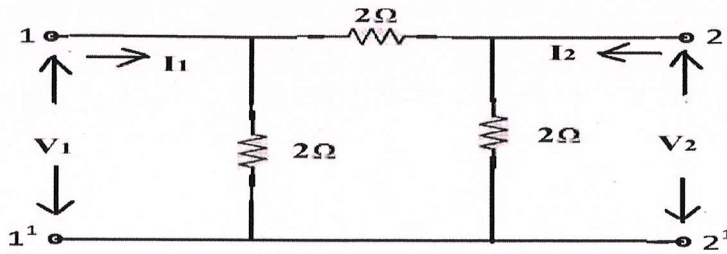
**UNIT-IV**

- 8 a Explain about Impedance parameters. 6M
- b Find the transmission parameters for the circuit shown in figure. 4M




OR

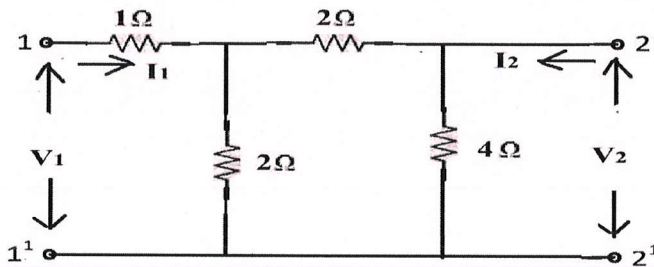- 9 a Explain about short-circuit parameters 5M
- b Find the h-parameters of the network shown in figure 5M



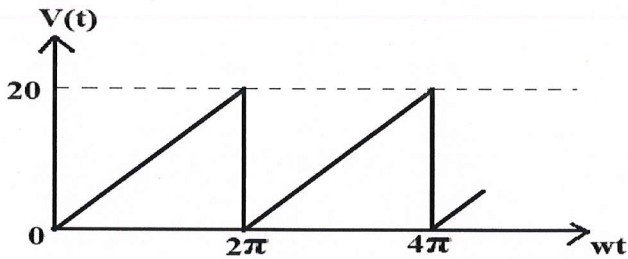
**UNIT-V**

- 10 a Derive the Trigonometric form of Fourier series. 5M
- b Find the Fourier series for the following waveform. 5M



OR

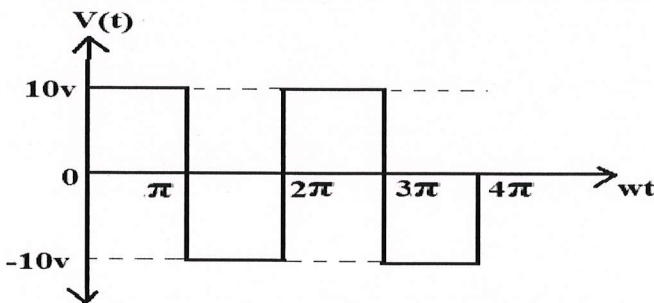- 11 a Derive the Exponential form of Fourier series 5M
- b Obtain the Fourier series for the following waveform shown in figure. 5M



\*\*\*END\*\*\*

