

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations August-2021

ELECTRONIC DEVICES AND CIRCUITS

(Common to EEE & ECE)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

**UNIT-I**

- 1 a The reverse saturation current of a silicon PN junction diode is  $10\mu\text{A}$ . Solve the diode current for the forward bias voltage of  $0.6\text{V}$  at  $25^\circ\text{C}$ . **5M**  
b Demonstrate the effect of temperature on V-I characteristics of PN junction diode. **7M**

**OR**

- 2 a Explain Positive and Negative Diode Clippers with neat waveforms. **6M**  
b What is a Clamper circuit? Describe about positive and negative clampers with neat circuit diagrams. **6M**

**UNIT-II**

- 3 a Draw the circuit diagram of a Half wave rectifier and explain its operation with the help of waveforms. **5M**  
b Determine the expressions for Average DC current, Average DC Voltage, RMS Value of Current, DC Power Output and AC Power input of a Half Wave Rectifier. **7M**

**OR**

- 4 a Demonstrate the working and characteristics of UJT with neat diagram. **6M**  
b Explain with diagram the construction, working and applications of Solar Cell. **6M**

**UNIT-III**

- 5 a Illustrate the Input and Output characteristics of BJT in CC Configuration. Also obtain the expression for Output collector current equation for a Transistor in CC configuration. **6M**  
b With a neat diagram, Explain how a transistor acts as an amplifier? **6M**

**OR**


- 6 Explain the construction and working principle of N-channel JFET. **12M**

**UNIT-IV**

- 7 a Explain Sensistor Compensation Technique. **5M**  
b Estimate the condition for achieving Thermal Stability. **7M**

OR

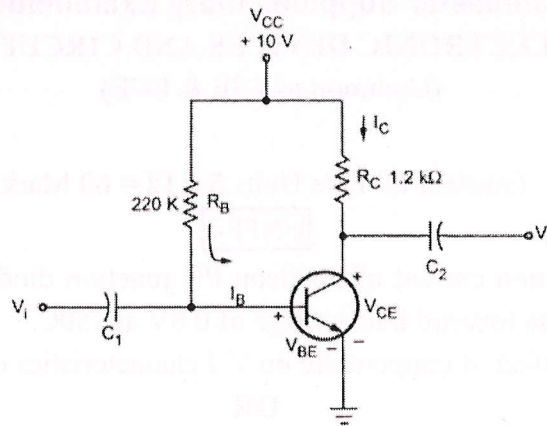- 8 a For the circuit shown in the Figure, solve  $I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_B$ ,  $V_C$  and  $V_{BC}$ . Assume that  $V_{BE} = 0$  and  $\beta = 50$ . 6M



- b Interpret Diode Compensation Techniques for the parameters  $V_{BE}$  and  $I_{CO}$ . 6M

**UNIT-V**

- 9 Using low frequency h-parameter model, Deduct the expressions for voltage gain, current gain, input impedance and output admittance for a BJT Amplifier in CE configuration. 12M

OR

- 10 a Determine the parameters  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_0$  of Common Collector Amplifier using simplified hybrid model analysis. 6M
- b A voltage source of internal resistance,  $R_s = 900\Omega$  drives a CC amplifier using load resistance  $R_L = 2000\Omega$ . The CE h parameters are  $h_{fe} = 60$ ,  $h_{ie} = 1200\Omega$ ,  $h_{oe} = 25\mu A/V$  and  $h_{re} = 2 \times 10^{-4}$ . Solve  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_0$  using approximate analysis. 6M

\*\*\* END \*\*\*