

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations August-2021

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Mechanical Engineering)

Time: 3 hours


Max. Marks: 60

(Answer all Six Units 6 X 10 = 60 Marks)

PART- A

UNIT-I

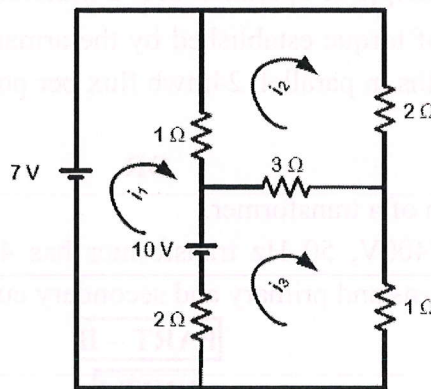- Q.1** a State and prove Kirchoff's laws with suitable examples. 5M
 b Find i_1, i_2, i_3 for the given circuit by using Kirchoff's laws? 5M




OR

- Q.2** Explain in detail about 10M
 (i) RMS value, (ii) Average value, (iii) Form factor, (iv) Peak factor
 (v) Prove that the form factor of the sinusoidal wave is 1.11.

UNIT-II

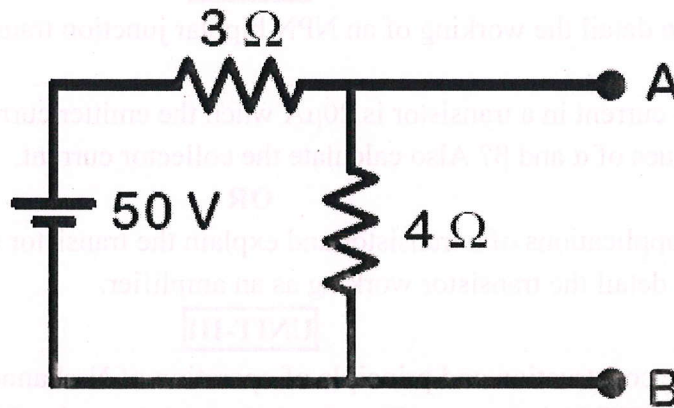
- Q.3** a State Norton's theorem. 2M
 b Find Norton's equivalent circuit across AB for the circuit shown. 8M



OR

Q.4 Find the Open circuit parameters for the given circuit

10M

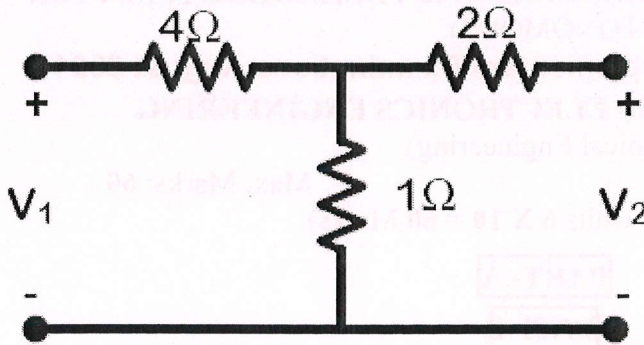

UNIT-III

- Q.5 a Discuss about the principle of operation of DC motors. 5M
 b Calculate the value of torque established by the armature of a 4-pole DC motor having 774 conductors, 2 paths in parallel, 24mwb flux per pole when the total armature current is 50A. 5M

OR

- Q.6 a Derive EMF equation of a transformer. 5M
 b A 100 kVA, 11000/400V, 50 Hz transformer has 40 secondary turns. Calculate the number of primary turns and primary and secondary currents. 5M

PART - B

UNIT-I

- Q.7 a With neat diagram, explain the working principle of Full Wave Rectifier. Draw its input and output waveforms. 5M
 b Derive the expression for Ripple factor and Efficiency of Full Wave Rectifier. 5M

OR

- Q.8 a Discuss Zener Diode breakdown mechanism. 5M
 b Draw the Zener diode in its reverse bias and explain its Volt-Ampere characteristics. 5M

UNIT-II

- Q.9 a Describe in detail the working of an NPN bipolar junction transistor. Why is it called Bipolar? 5M
 b If the base current in a transistor is $20\mu\text{A}$ when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current. 5M

OR

- Q.10 a Write the applications of a transistor and explain the transistor acts a switch. 5M
 b Explain in detail the transistor working as an amplifier. 5M

UNIT-III

- Q.11 a Explain the construction and principle of operation of N-channel JFET. 5M
 b Define the JFET Volt-Ampere Characteristics and determine FET parameters. 5M

OR

- Q.12 a Explain the static characteristics of MOSFET and draw its characteristics 5M
 b Write the application of MOSFET 5M

*** END ***