

Reg. No:

--	--	--	--	--	--	--	--	--	--

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

B.Tech II Year I Semester Supplementary Examinations August-2021

**NETWORK THEORY
(Electronics & Communication Engineering)**


Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)


UNIT-I

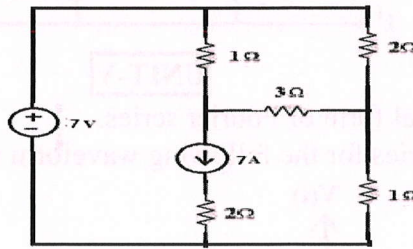- 1 a State and prove Reciprocity theorem. 6M
 b Determine the mesh currents for the circuit shown in below figure. 6M



OR

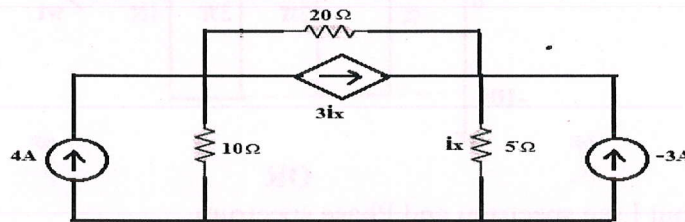- 2 a Explain about Nodal analysis and write the steps for applying nodal analysis. 6M
 b Determine i_x for the following network. 6M




UNIT-II

- 3 a A series RLC circuit has $R=10\Omega$, $L=0.1H$ and $C=50\mu F$. The applied voltage is 100V. Find Resonant frequency & Quality factor of a coil. 6M
 b Explain about Parallel resonance with phasor diagrams. 6M

OR

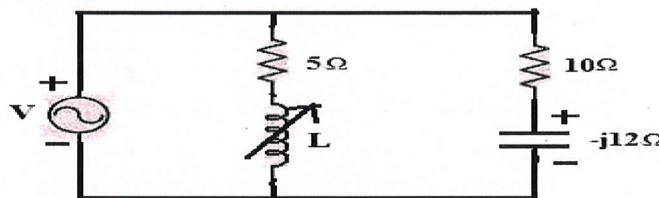- 4 a Explain about Quality factor and Band-width of Series resonance. 6M
 b Find the value of "L" at which the circuit resonates at a frequency of 1000 rad/sec in the circuit shown in figure 6M



UNIT-III

- 5 a Derive the Laplace Transform of Series RC Circuit. 6M
 b The Circuit Consists Of Resistance=20 Ohm, Inductance = 0.05H, Capacitance = 20uF in Series with a 100V Constant at $t=0$. Find The Current Transient. 6M

OR


- 6 Derive the Transient Response of series RLC-circuit with D.C excitation. 12M

UNIT-IV

- 7 a Derive the expressions for Z-parameters in terms of ABCD-parameters. 6M
 b The hybrid parameters of a two-port network is shown in figure are, $h_{11} = 1K$, $h_{12} = 0.003$, $h_{21} = 100$ and $h_{22} = 50\mu\Omega$. Find V_2 and Z-parameters of the network. 6M


OR

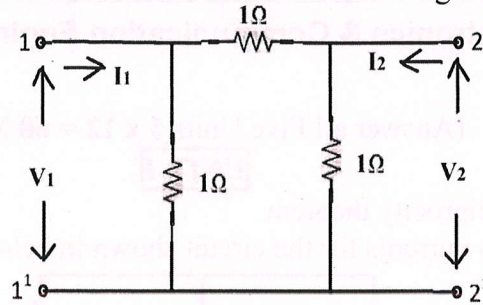- 8 a Explain about ABCD-parameters. 6M
 b Find the Z-parameters of the network shown in below figure. 6M



UNIT-V

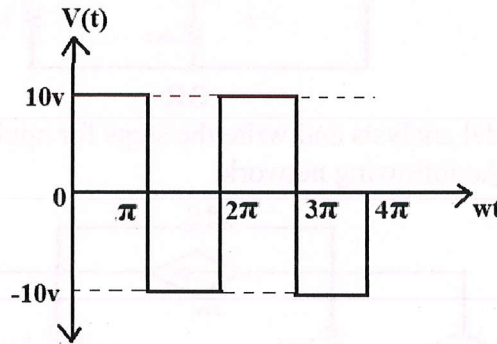- 9 a Derive the Exponential form of Fourier series. 6M
 b Obtain the Fourier series for the following waveform shown in figure. 6M



OR

- 10 a Explain about Line spectrum and Phase spectrum. 6M
 b Explain about waveform symmetry for even and odd functions. 6M

*** END ***