

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)
B Tech II Year I Semester Supplementary Examinations August-2021
BASIC ELECTRONIC DEVICES
(Common to ECE & EEE)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a With neat diagrams, explain forward and reverse biasing of a PN Junction diode. 6M
b Write notes on Diode Resistance. 6M

OR

- 2 a What is transition capacitance? Derive the expression for transition capacitance of a PN Junction Diode. 6M
b Mention the importance of Diffusion capacitance. Derive the expression for Diffusion capacitance of a PN Junction Diode. 6M

UNIT-II

- 3 a Draw and explain VI characteristics of Tunnel Diode. 8M
b Discuss the energy band structure of a Tunnel Diode. 4M

OR

- 4 Draw the basic structure of an SCR. Explain its characteristics and list the Applications 12M

UNIT-III

- 5 a With neat diagram, explain Bridge Rectifier 6M
b A bridge rectifier uses four identical diodes having forward resistance of 5Ω each. Transformer secondary resistance is 5Ω and the secondary voltage of 30V (rms). Determine the DC output voltage for $I_{DC} = 200\text{mA}$ and the value of the ripple voltage. 6M

OR

- 6 a Draw the circuit of capacitor filter and explain its operation. 5M
b Derive the expression for ripple factor of HWR and FWR with capacitor filter. 7M

UNIT-IV

- 7 a With a neat diagram, explain how a transistor acts as an amplifier? 6M
b Discuss the Input and Output characteristics of BJT in CC Configuration 6M

OR

- 8 a Discuss the Input and Output characteristics of BJT in CC Configuration 6M
b Give the comparison between JFET and MOSFET. 6M

UNIT-V

- 9 a Define Transistor Biasing and explain the need for Biasing? 6M
b Explain the concept of DC and AC Load lines and discuss the criteria for fixing the Q-point. 6M

OR

- 10 a Explain Collector to Base bias of a Transistor with neat circuit diagram 6M
b Describe the factors to be considered while designing the biasing circuit which are responsible for shifting the operating point. 6M

*** END ***