

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year I Semester Supplementary Examinations August-2021

NETWORK ANALYSIS & SYNTHESIS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units 5 x 12 = 60 Marks)

UNIT-I

- 1 a Derive the relationship of voltage and current in star connected load. **6M**
 b A three phase balance delta connected load of $(4+j8) \Omega$ is connected across a 400V, 3 ϕ balanced supply. Determine the phase currents and line currents. And also power drawn by the load. Assume RYB phase sequence. **6M**

OR

- 2 a Three impedances $Z_1=20 \angle^{30^\circ}$, $Z_2=40 \angle^{60^\circ}$, $Z_3=10 \angle^{-90^\circ}$ are delta connected to a 400V, 3 ϕ System. Determine i) phase currents ii) line currents iii) total power consumed by the load. **6M**
 b An unbalanced 4 wire star connected load has a balanced voltage of 400V. The load are $Z_1=(4+j8) \Omega$, $Z_2=(5+j4) \Omega$, $Z_3=(15+j20) \Omega$. Calculate line currents, current in neutral wire, total power. **6M**

UNIT-II


- 3 a Derive the transient response of an RC circuit with DC excitation. **8M**
 b A series RL circuit with $R=30\Omega$ and $L=15H$ has a constant voltage $V=60V$ applied at $t=0$. Determine the current I , the voltage across the resistor and across the inductor. **4M**

OR

- 4 a Derive the transient response of an RLC circuit with sinusoidal excitation. **10M**
 b Define time constant **2M**


UNIT-III

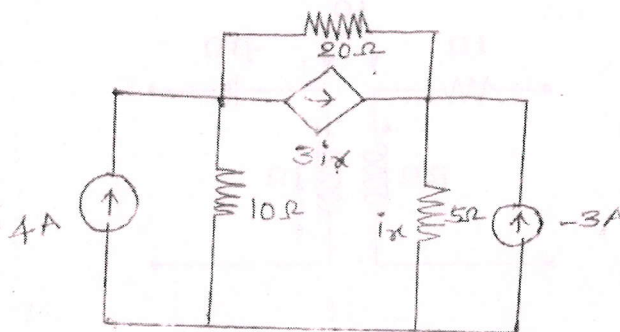- 5 a Define tree, co-tree and planar graphs **4M**
 b Determine i_x for the following network using network topology. **8M**




OR

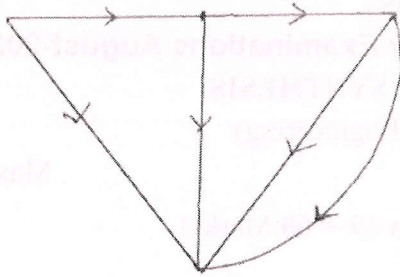6 a Find the tie-set for the following oriented graph: 5M




b Draw the dual network: 7M

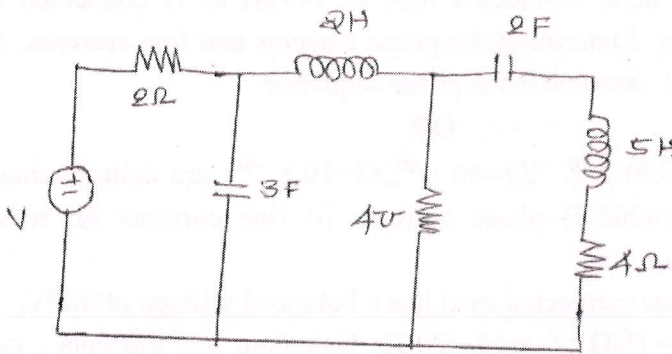

UNIT-IV

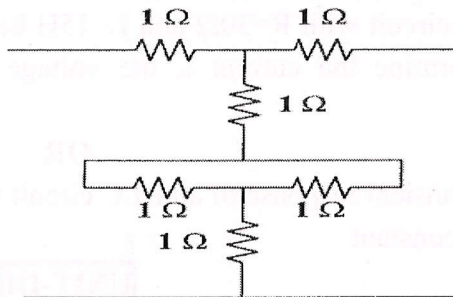
7 a Determine the Z parameters of the following two port network. 10M



b Mention the condition for symmetry and reciprocity in y-parameters: 2M

OR

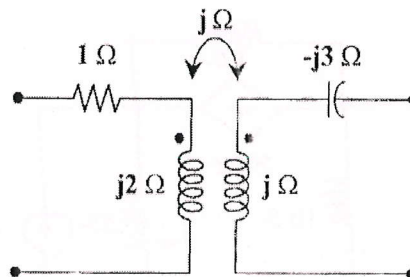8 a Obtain the T parameters of the following two port network 8M



b Derive the expressions for h-parameters of a two port network? 4M

UNIT-V

- 9 a Explain about different types of filters. **6M**
b Design a π -type attenuator to give 10 dB attenuation and to have a characteristic impedance of 200 Ohms. **6M**

OR

- 10 a Design a high pass filter having cut of frequency of 1KHz with load resistance of 600ohms. **6M**
b Explain about constant K low pass filter. **6M**

*** END ***