

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations July-2021

DIGITAL ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

PART-A

(Answer all the Questions 5 x 2 = 10 Marks)

- | | | | |
|---|---|---|----|
| 1 | a | Convert the following to gray code. $(10110011)_2$ | 2M |
| | b | Define Multiplexer. | 2M |
| | c | What is the difference between Latch and Flip – flop? | 2M |
| | d | Define FAN IN and FAN OUT. | 2M |
| | e | What are the different types of semiconductor memories? | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | |
|---|---|---|----|
| 2 | a | Convert the following to Decimal and then to Octal
i) $(10110011)_2$ ii) $(1234)_{16}$ | 5M |
| | b | Perform the subtraction by using 1's complement for the given $(10101 - 11011)$. | 5M |

OR

- | | | | |
|---|---|--|----|
| 3 | a | Explain Different Types of binary codes and give the examples. | 5M |
| | b | Simplify the following Boolean expressions:
i) $F = (A+B)(A'+C)(B+C)$. ii) $F = XY+XYZ+XYZ'+X'YZ$ | 5M |

UNIT-II

- | | | | |
|---|---|--|----|
| 4 | a | Minimize the following Boolean function using K-Map
$F(A, B, C, D) = \sum m(0, 2, 4, 6, 8, 10, 12, 14)$. | 5M |
| | b | What is Decoder? design 3:8 decoder. | 5M |

OR

- | | | | |
|---|---|---|----|
| 5 | a | Minimize the given Boolean function $F(A,B,C,D) = \sum m(0,1,2,3,6,7,13,15)$ using tabulation method. | 5M |
| | b | Design 2-bit comparator with Logic diagram. | 5M |

UNIT-III

- | | | | |
|---|---|--|----|
| 6 | a | Design D Flip Flop by using SR Flip Flop Explain the operation with truth table. | 6M |
| | b | Write the differences between combinational and sequential circuits. | 4M |

OR

- | | | | |
|---|---|---|----|
| 7 | a | Explain working of Master Slave Flip flop with neat diagram. | 5M |
| | b | Design T Flip Flop by using JK Flip Flop and draw the timing diagram. | 5M |

UNIT-IV

- | | | |
|---|--|-----|
| 8 | Perform the analysis of standard TTL NAND gate and give its characteristics. | 10M |
|---|--|-----|

OR

- | | | |
|---|--|-----|
| 9 | Explain about TTL to CMOS interfacing. | 10M |
|---|--|-----|

UNIT-V

- | | | |
|----|---|-----|
| 10 | Implement the following Boolean function using PLA
i) $F(w,x,y,z) = \sum m(0,1,3,5,9,13)$ ii) $F(w,x,y,z) = \sum m(0,2,4,5,7,9,11,15)$ | 10M |
|----|---|-----|

OR

- | | | |
|----|---|-----|
| 11 | What is ROM organization? Explain about Different types of ROM. | 10M |
|----|---|-----|

END