

Reg. No: 

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR  
(AUTONOMOUS)

B.Tech II Year II Semester Supplementary Examinations July-2021

POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 60

**PART-A**

(Answer all the Questions 5 x 2 = 10 Marks)

- |   |   |    |
|---|---|----|
| 1 | a Define Latching current.  | 2M |
|   | b Define Transformer utilization factor.                          | 2M |
|   | c What is meant by step-down chopper?                             | 2M |
|   | d What are the different methods for forced commutation employed? | 2M |
|   | e What is meant by VSI?   | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |   |  |    |
|---|--|----|
| 2 | a Explain V-I Characteristics Of Diode.                        | 5M |
|   | b Necessity Of Commutation, What are the Types Of Commutation? | 5M |

**OR**

- |   |  |     |
|---|--|-----|
| 3 | Briefly explain about insulated gate bipolar transistor (IGBT) and it's switching characteristics. | 10M |
|---|--|-----|

**UNIT-II**

- |   |  |     |
|---|--|-----|
| 4 | Explain the operation of Three phase fully controlled rectifier with RL load and also derive the average and RMS load voltage. | 10M |
|---|--|-----|

**OR**

- |   |  |     |
|---|--|-----|
| 5 | A single phase half wave converter is operated from a 230V, 50Hz supply. If the load is Resistive of value 10 ohms and firing angle is 60° Determine i) the rectification efficiency ii) form factor iii) ripple factor iv) Transformer utilization factor v) Peak inverse voltage of thyristor. | 10M |
|---|--|-----|

**UNIT-III**

- |   |   |     |
|---|---|-----|
| 6 | Derive the expression for output voltage of step down chopper with neat diagrams. | 10M |
|---|---|-----|

**OR**

- |   |   |     |
|---|---|-----|
| 7 | The boost converter has an input voltage of $E_{dc}=5V$ . the required average output voltage is $E_0=15V$ And the average load current $I_0=0.5A$ . The switching frequency is 25 kHz. If the $L=150\mu H$ and $C=220\mu F$ , determine (a) the duty cycle (b) the ripple current of inductor $\Delta I$ (c) the peak current of inductor $I_2$ , (d) The ripple voltage of filter capacitor $\Delta V_C$ , and (e) the critical values of $L$ and $C$ . | 10M |
|---|---|-----|

**UNIT-IV**

- |   |   |     |
|---|---|-----|
| 8 | Analyze the single-phase half bridge Voltage Source Inverter and perform steady state analysis? | 10M |
|---|---|-----|

**OR**

- |   |   |     |
|---|---|-----|
| 9 | Explain briefly single pulse width modulation with neat diagrams. | 10M |
|---|---|-----|

**UNIT-V**

- 10 Explain the three-phase Voltage Source Inverter with  $120^\circ$  conduction mode .Also **10M**  
derive the output voltage, output current.
- OR**
- 11 1- $\emptyset$  half bridge inverter has a resistive load of  $R= 3\Omega$ ,and the d.c input voltage **10M**  
 $E_{dc}=50V$ .calculate i)RMS output voltage at the fundamental frequency  $E_1$ . (ii) the  
output power  $P_0$  (iii) the average and peak current of each thyristor and (iv) the peak  
reverse –blocking voltage of each thyristor.

\*\*\*END\*\*\*