

Reg. No:

--	--	--	--	--	--	--	--	--	--

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech II Year II Semester Regular Examinations July-2021

ELECTRONIC CIRCUIT ANALYSIS

(Electronics and Communication Engineering)

Time: 3 hours

Max. Marks: 60

(Answer all Five Units **5 x 12 = 60** Marks)

UNIT-I

- 1 a Sketch the Hybrid-pi model and explain the significance of each and every component in it. L3 6M
- b Short circuit CE current gain of a transistor is 25 at a frequency of 2MHz. If $f_{\beta} = 200\text{KHz}$, calculate (i) f_T (ii) h_{fe} (iii) Find $|A_i|$ at frequency of 10MHz and 100MHz. L3 6M

OR

- 2 a Construct the block diagram of n-stage cascaded amplifier and analyze its various parameters. L3 8M
- b Define Darlington Pair and list its applications. L1 4M

UNIT-II

- 3 a Explain the basic concept of Feedback in amplifier with suitable block diagram. L2 8M
- b List the characteristics of negative feedback amplifiers. L1 4M

OR

- 4 a An RC coupled amplifier has a mid-frequency gain of 200 and a frequency response from 100 Hz to 20 KHz. A negative feedback network with $\beta = 0.02$ is incorporated into the amplifier circuit. Estimate the new system performance. L5 6M
- b Compare various types of feedback amplifiers. L4 6M

UNIT-III

- 5 a Establish the condition for oscillation with suitable diagram. L3 5M
- b Construct RC phase shift oscillator using BJT and deduce its expression for frequency of oscillations. L4 7M

OR

- 6 a Explain working of Crystal oscillator and deduce the expression for frequency of oscillations. L4 8M
- b In the Colpitts oscillator, $C_1 = 0.2\mu\text{F}$ and $C_2 = 0.02\mu\text{F}$. If the frequency of oscillation is 10kHz, Calculate the value of inductor. L3 4M

UNIT-IV

- 7 a Discuss about Transformer coupled Class A Power Amplifier with diagram L3 6M
and determine its Maximum efficiency.
- b A Class B push pull amplifier drives a load of 18Ω , connected to the L3 6M
secondary of ideal transformer. The V_{CC} is 25V. If number of turns on
primary is 150 and secondary is 50. Determine maximum power output,
DC power input and efficiency.

OR


- 8 a Explain the effect of cascading single tuned amplifiers on bandwidth. L2 6M
- b With circuit diagram, describe the stagger tuning operation. Sketch L3 6M
necessary graph.

UNIT-V

- 9 a What is a Monostable multivibrator? Explain its working with the help of L2 7M
waveforms.
- b Compare Astable and Monostable multivibrators. L4 5M

OR

- 10 a Explain a triggering method for Bistable multivibrator. L2 6M
- b Calculate the stable state currents and voltages for the bistable multivibrator L4 6M
having $V_{CC} = 12\text{ V}$, $V_{BB} = -12\text{ V}$, $R_{C1} = R_{C2} = 2.2\text{ k}\Omega$, $R_1 = R_2 = 15\text{ k}\Omega$,
 $R_3 = R_4 = 100\text{ k}\Omega$, $C_1 = C_2 = 0.1\text{ }\mu\text{F}$. Assume that a transistor having a
minimum hfe of 20 is used.

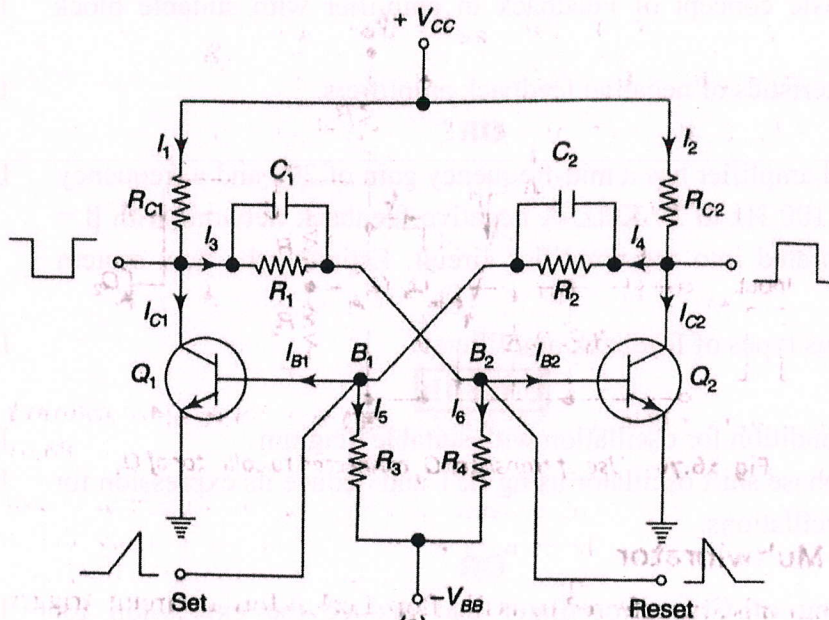

*** END ***